



VISUAL
PHYSICS

SHORT NOTES

C H A P T E R

Alternating Current



+91 999021287





www.visualphysics.in



GET IT ON

Google Play

Alternating Current

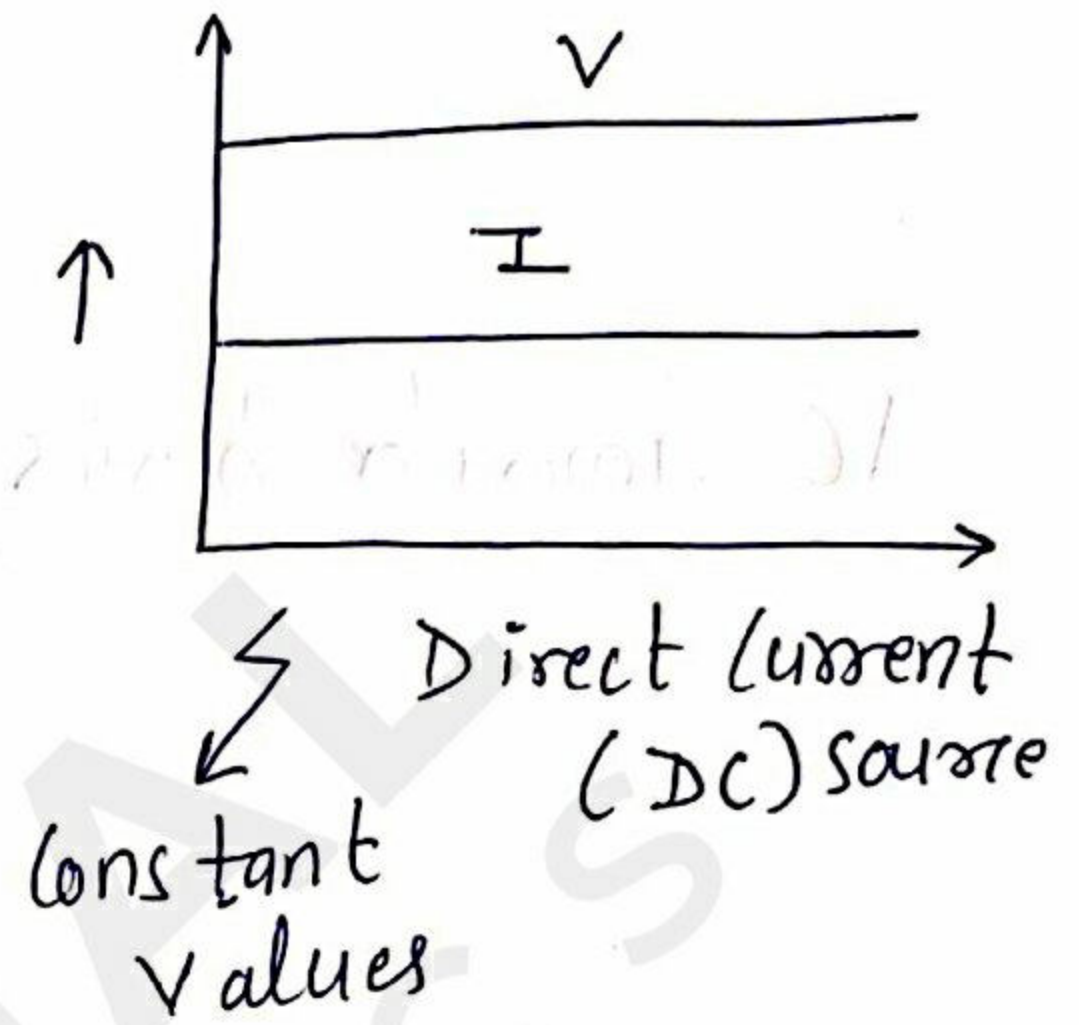
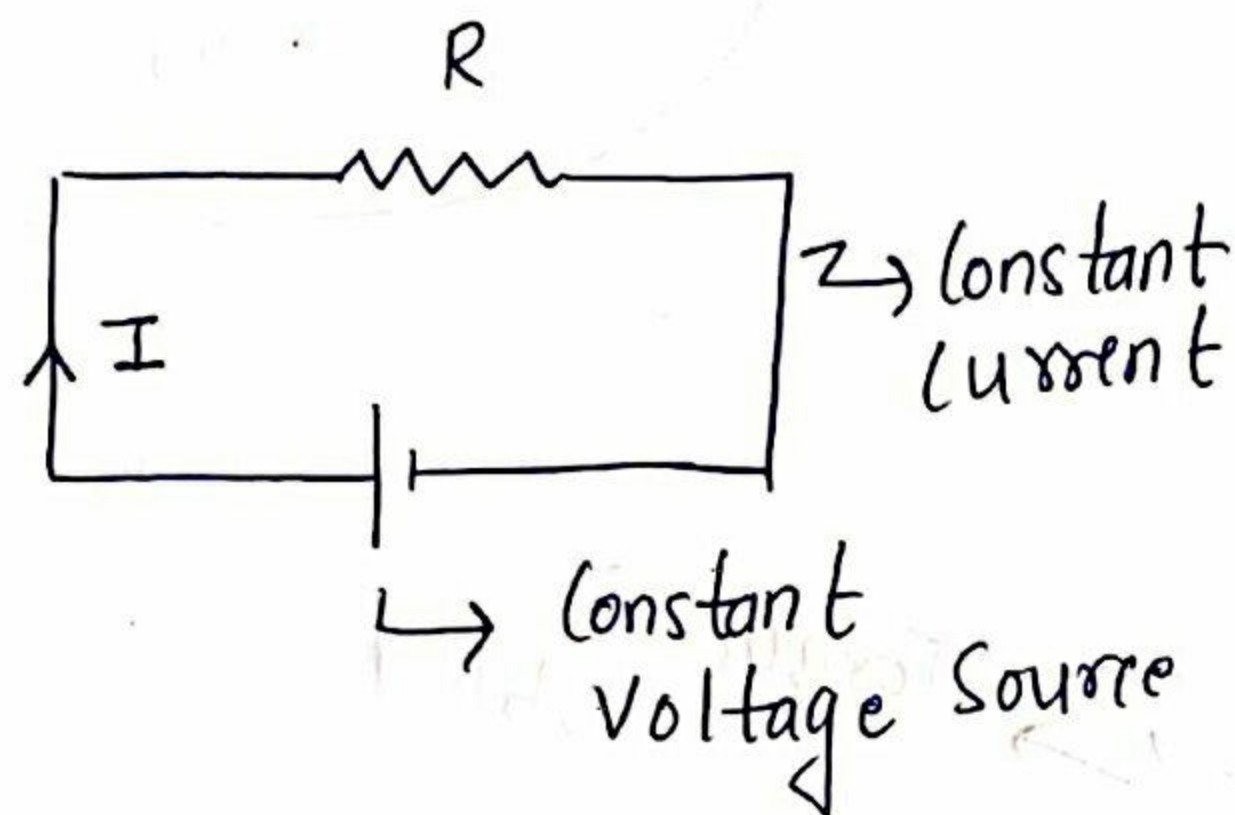


Generally,

current sources, are not having constant voltage & current.

In constant (DC) source $\rightarrow$ electrons move from one point to other.

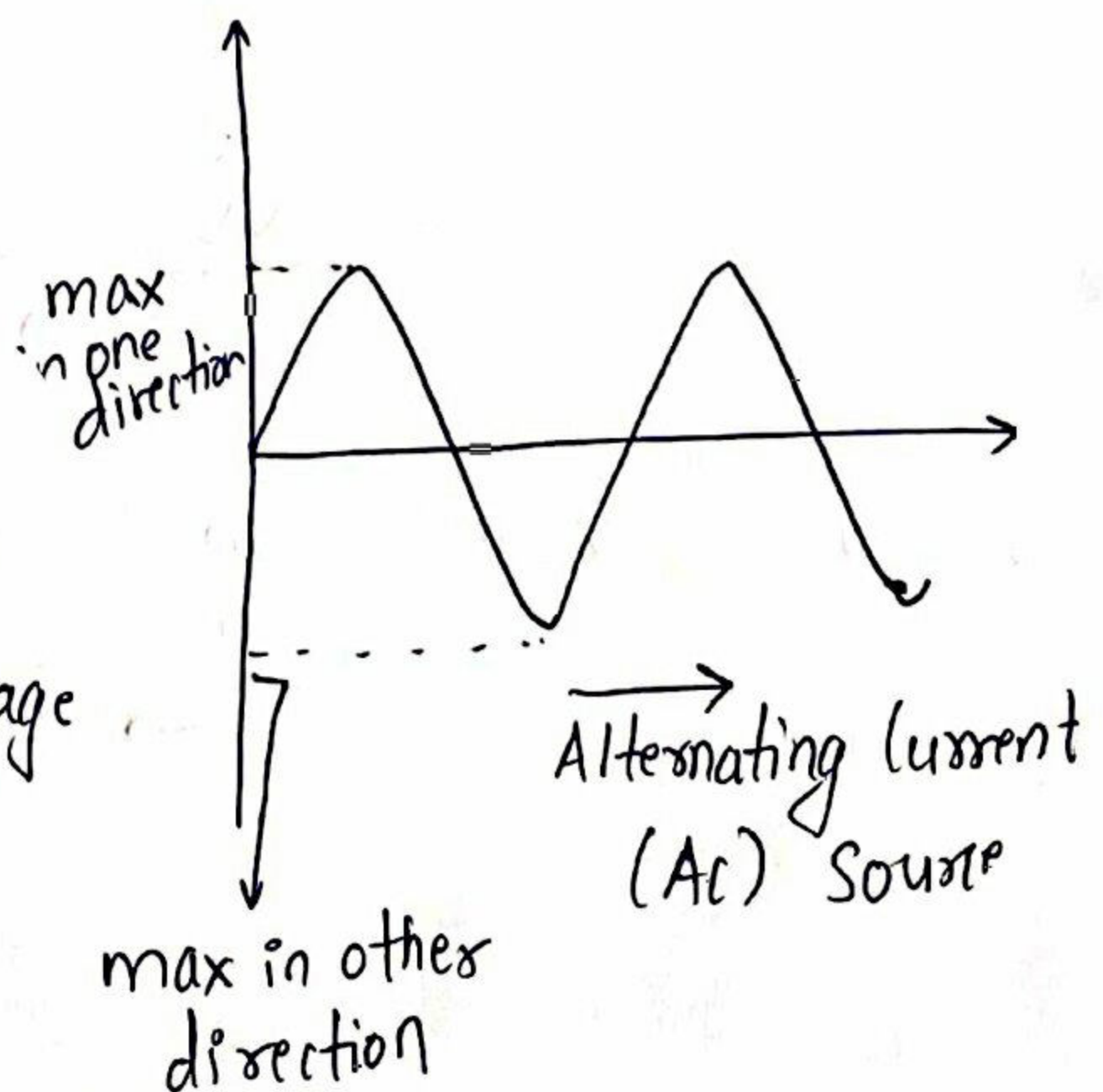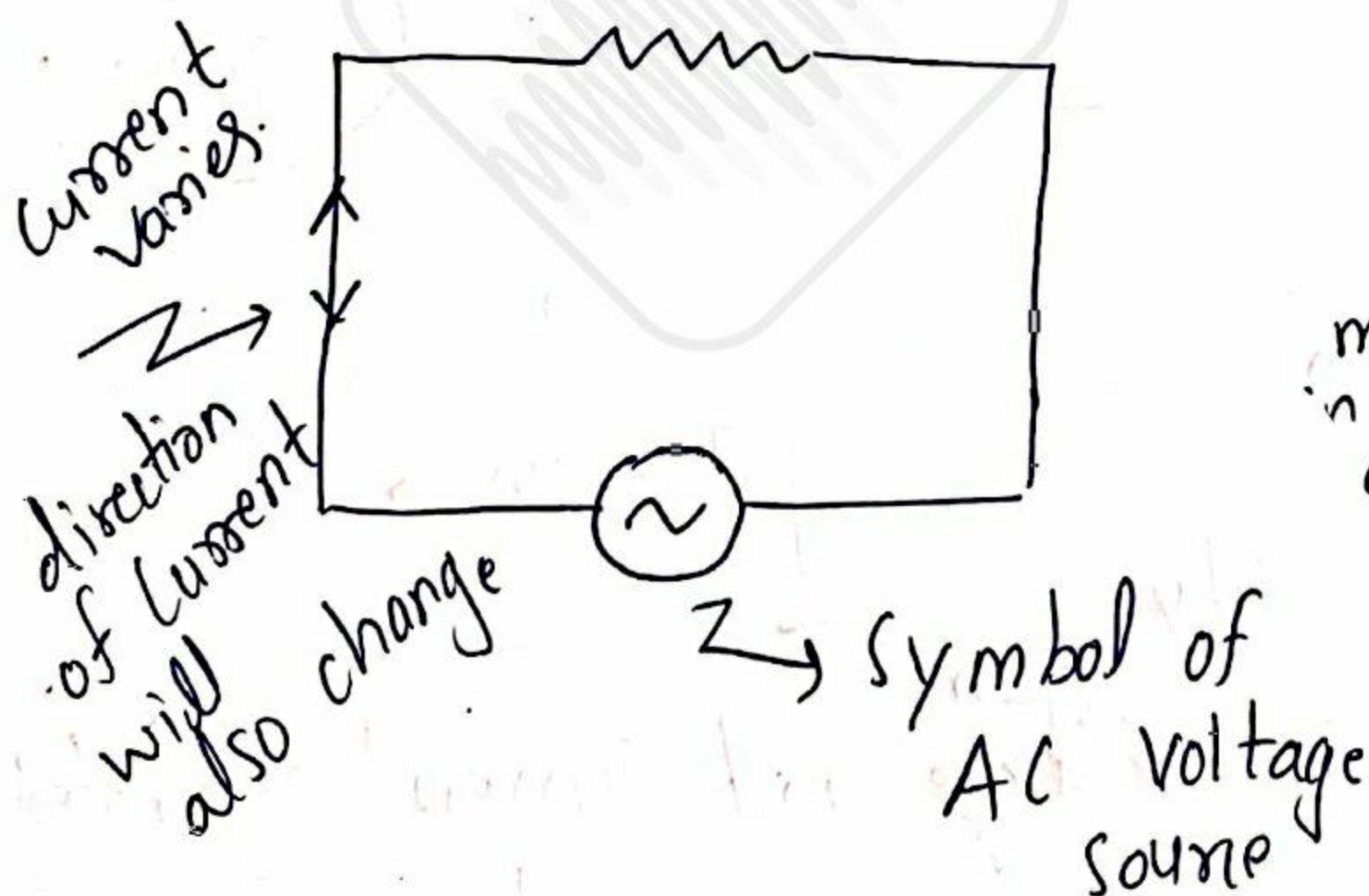
In Alternating Source (AC) $\rightarrow$ electrons oscillate, they don't move around much.



AC $\rightarrow$ easy and economical to generate, hence in homes we get AC.

$\rightarrow$ And can be effectively transmitted over distance

AC Generator basics.

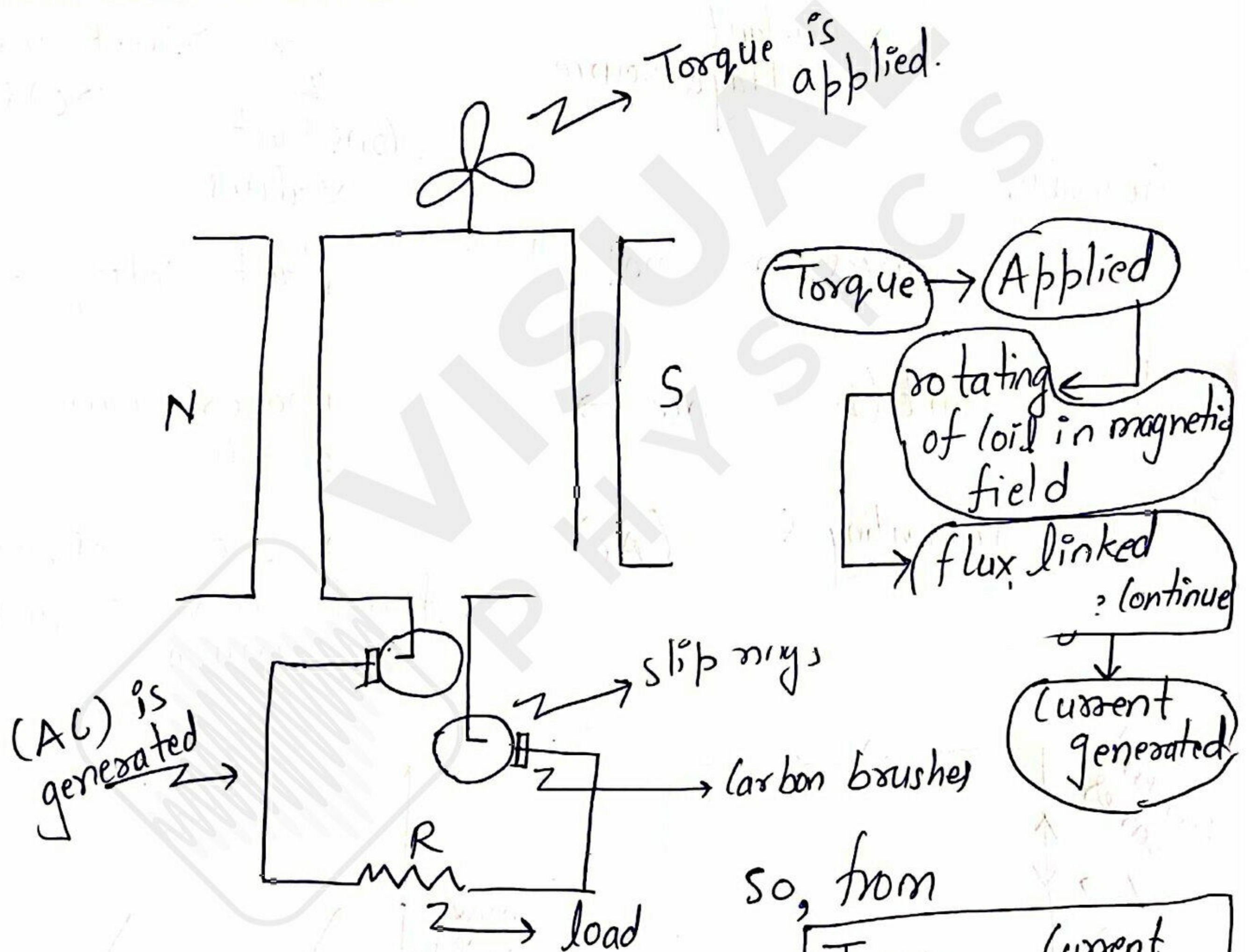

* As flux varies $\rightarrow$ sinusoidally

$\rightarrow$ So emf and current generated sinusoidal.

and Current


So Voltage & Current can be represented by:

$$\begin{aligned} & \left\{ \begin{array}{l} V = V_0 \sin(\omega t + \phi_1) \\ i = i_0 \sin(\omega t + \phi_2) \end{array} \right\} \begin{array}{l} \phi_1, \phi_2 \text{ initial phase} \\ V_0, i_0 \rightarrow \text{amplitudes.} \end{array} \\ & \omega \rightarrow \text{angular frequency} \\ & \boxed{\omega = 2\pi f} \rightarrow \text{frequency} \end{aligned}$$

Similar as of SHM.

means, it can be represented
As projection of uniform circular motion

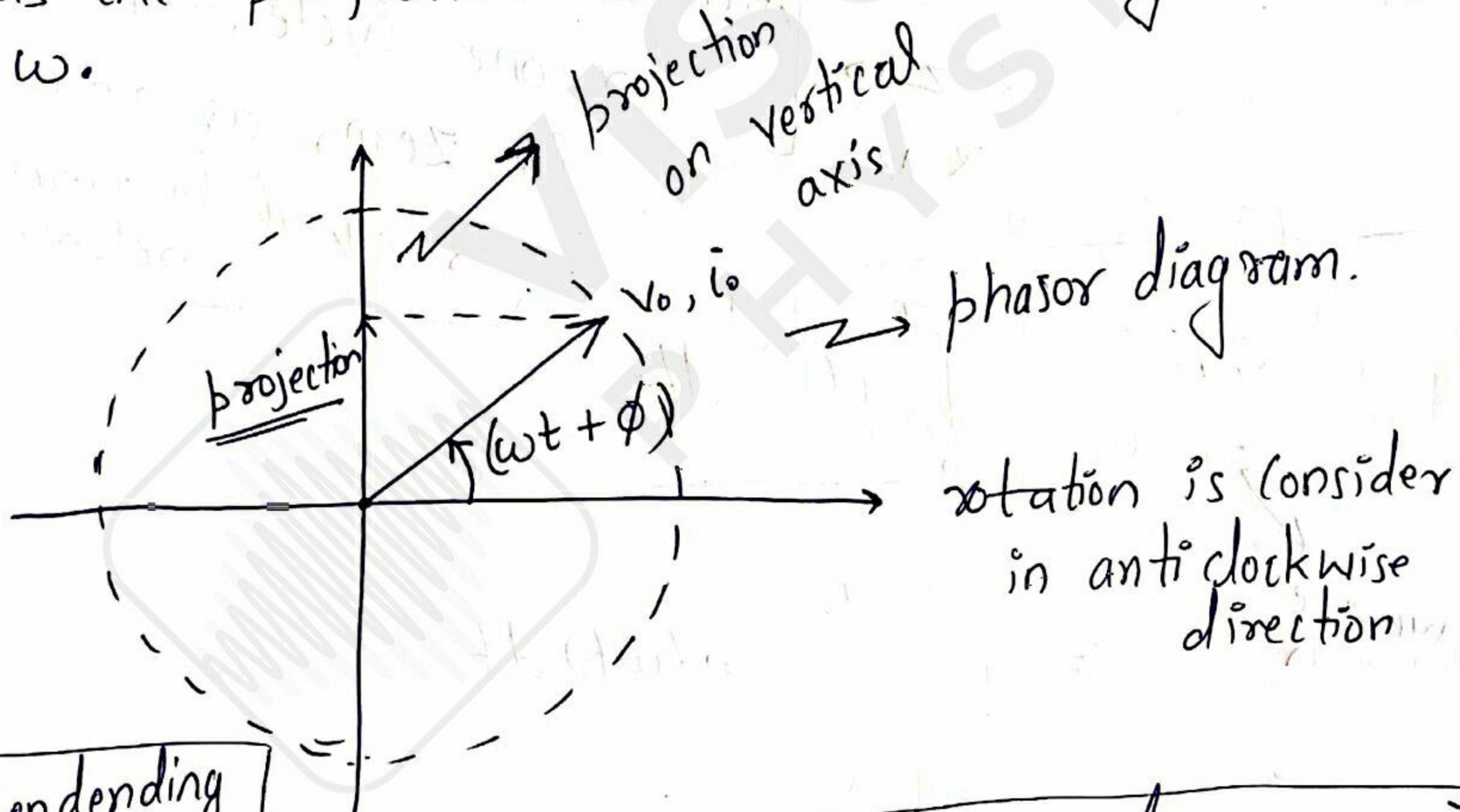So, we can similarly represent voltage and current as the projection of vector, with angular frequency ω .



dependending

on components, voltage and current are not necessary in

phase.


reaching max, min at same time.

if for example $V(t) = V_0 \sin(\omega t)$

and $i(t) = i_0 \sin(\omega t - \phi)$

i.e. $i \rightarrow \phi \text{ behind} \rightarrow v$

So represented as

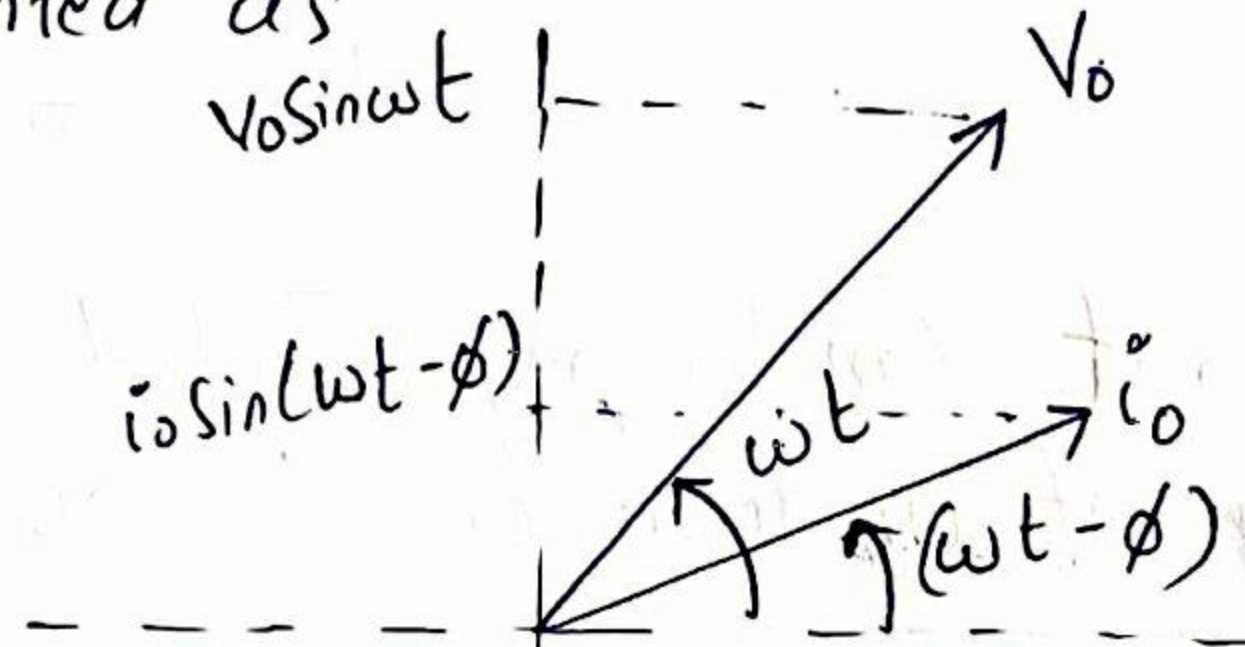

* V & i have same frequency but may or may not same amplitude

Area under i, v and t graph for one cycle, that is zero, as area above is equal to area below.

Average of i & v

$$\begin{aligned} \langle i(t) \rangle &= \frac{\int_0^T i(t) dt}{T} \\ &= \frac{i_0}{T} \int_0^T \sin(\omega t) dt \\ &= -\frac{i_0}{\omega T} [\cos \omega t - \cos 0] = 0 \end{aligned}$$

average of $i(t)$

similarly $\langle v(t) \rangle = 0$

average of $v(t)$

“so, in terms of dealing with AC components average values are not helpful.”

root means square.

let

i_{rms} $\rightarrow$ Constant current source value.
which provides same heat in one cycle
as the AC current $i(t)$ emits.

$$\text{as } H = \int_0^T i^2 R dt =$$

$$= \int_0^T i_0^2 \sin^2 \omega t R dt$$

$$H = \int_0^T i_{rms}^2 R dt$$

$$\Rightarrow i_{rms}^2 R T = \int_0^T i_0^2 \sin^2 \omega t R dt$$

$$= i_0^2 R \int_0^T \left[1 - \frac{\cos(2\omega t)}{2} \right] dt$$

$$i_{rms}^2 R T = \frac{i_0^2 R T}{2}$$

$$\boxed{i_{rms} = \frac{i_0}{\sqrt{2}}}$$

Now as from ohm's law

$$V(t) = i(t)R$$

We will get same result for rms value of voltage. rms value.

$$V_{rms} = \frac{V_0}{\sqrt{2}}$$

* AC voltmeter and ammeter are calibrated to measure the rms values.
"So if nothing is mentioned than values provided are in rms form unless stated."

so for calculation of peak value,


$$V_0 = \sqrt{2} V_{rms} \text{ and } i_0 = \sqrt{2} i_{rms}$$

* DC voltmeter & Ammeter cannot be used to measure values of AC, Voltage & Current.

as DC voltmeter and Ammeter measures average values

Zero for AC, Current and Voltage

Resistive load

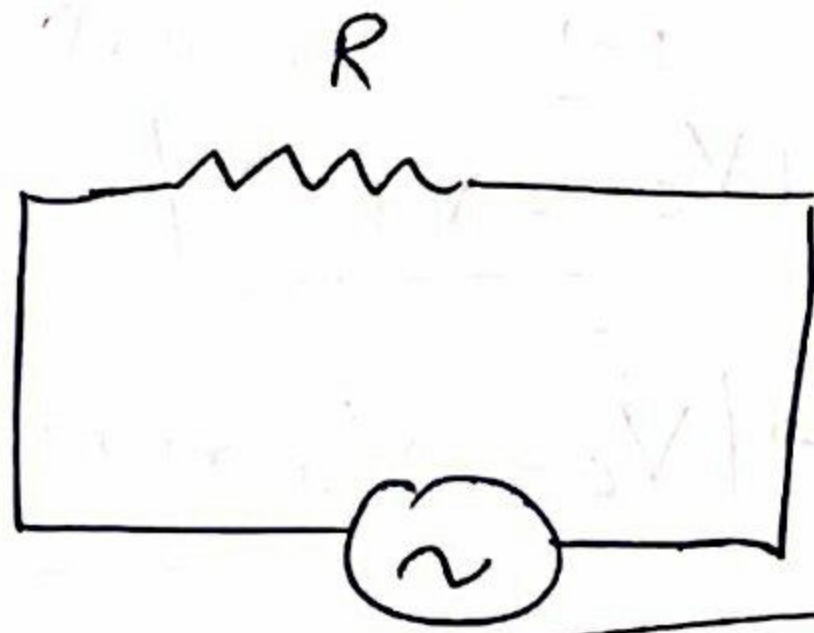

As, from ohm's law
around the resistor

$$\Rightarrow i(t) = \frac{V(t)}{R}$$

$$V(t) = V_0 \sin(\omega t)$$


$$\Rightarrow i(t) = \left(\frac{V_0}{R}\right) \sin \omega t$$

$$\Rightarrow i(t) = i_0 \sin \omega t$$

$$i_0$$

max value
of i

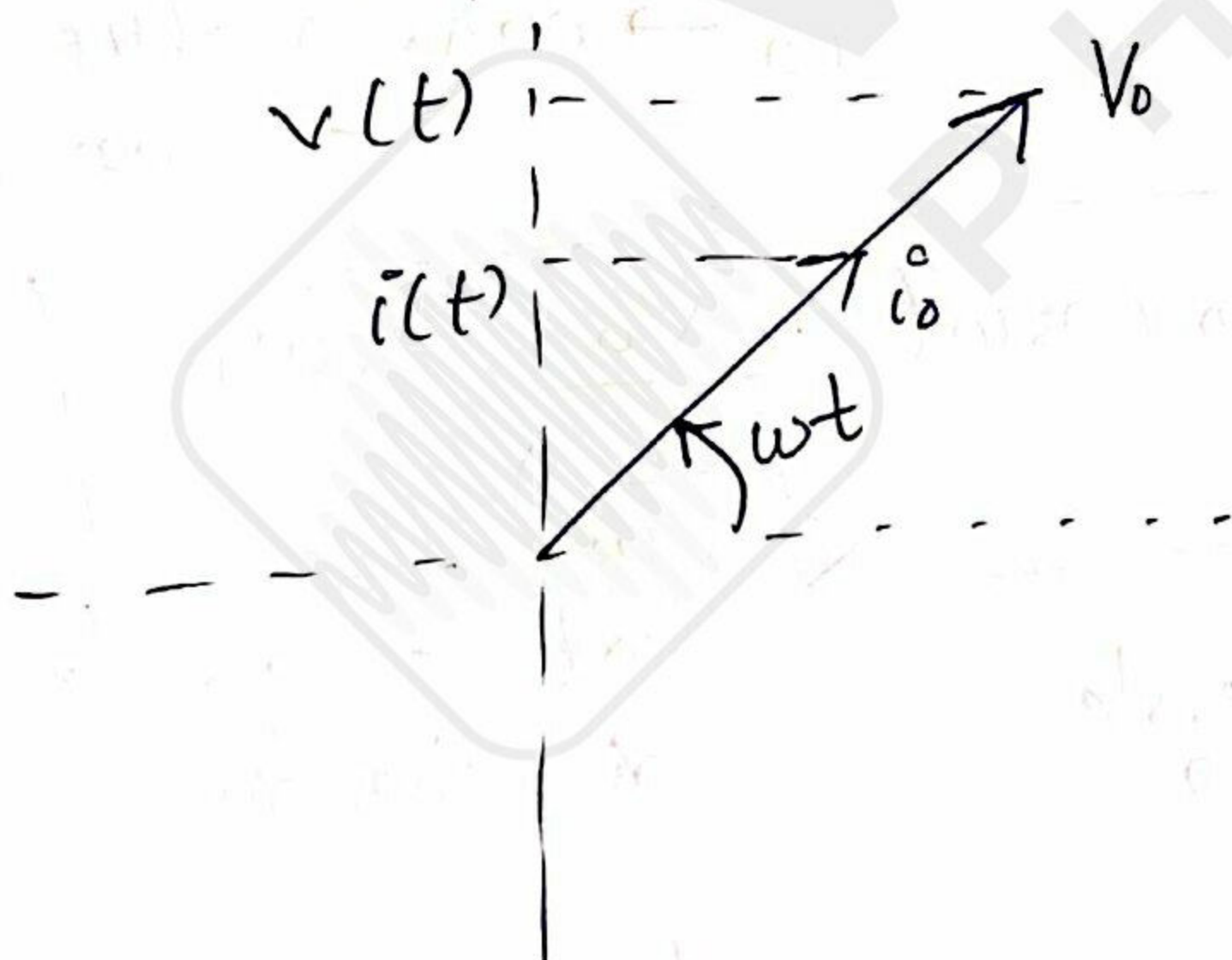
So, Voltage across resistor and Current through it are in same phase.



that is they achieve their max and min value at same time. And become zero at same time.

Capacitive load

Capacitor

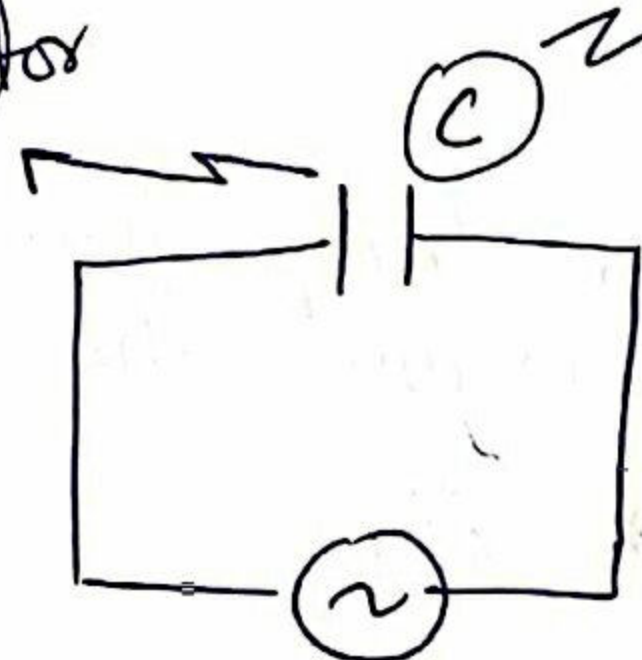

Capacitance

potential across capacitor

$$\text{so, } V_c = V(t)$$

$$\Rightarrow V_c = V_0 \sin \omega t$$

$$V(t) = V_0 \sin \omega t$$

As we know for capacitor

$$q(t) = C V_c$$

$$\Rightarrow q(t) = C V_0 \sin \omega t$$

now

$$i(t) = \frac{d}{dt} (q(t)) = (C V_0 \omega) \cos \omega t$$

$i_0 \rightarrow$ max value of current

Capacitive reactance

$$i(t) = i_0 \cos \omega t = \frac{V_0}{\left(\frac{1}{C\omega}\right)} \cos \omega t$$

Sort of resistance for capacitor

$$X_c = \frac{1}{\omega C}$$


[unit] = Resistance = Ω (ohm)

for $\omega \rightarrow 0$ (dc) $\rightarrow$ Open circuit
 $X_c \rightarrow \infty$, $i = 0$

$\omega \rightarrow \infty$
 $X_c \rightarrow 0$, $i \rightarrow \infty$ $\rightarrow$ Capacitor behave as short circuit

$\Rightarrow$ current through capacitor
 $i_c(t) = i_0 \sin(\omega t + \pi/2)$
 $V_c(t) = V_0 \sin \omega t$

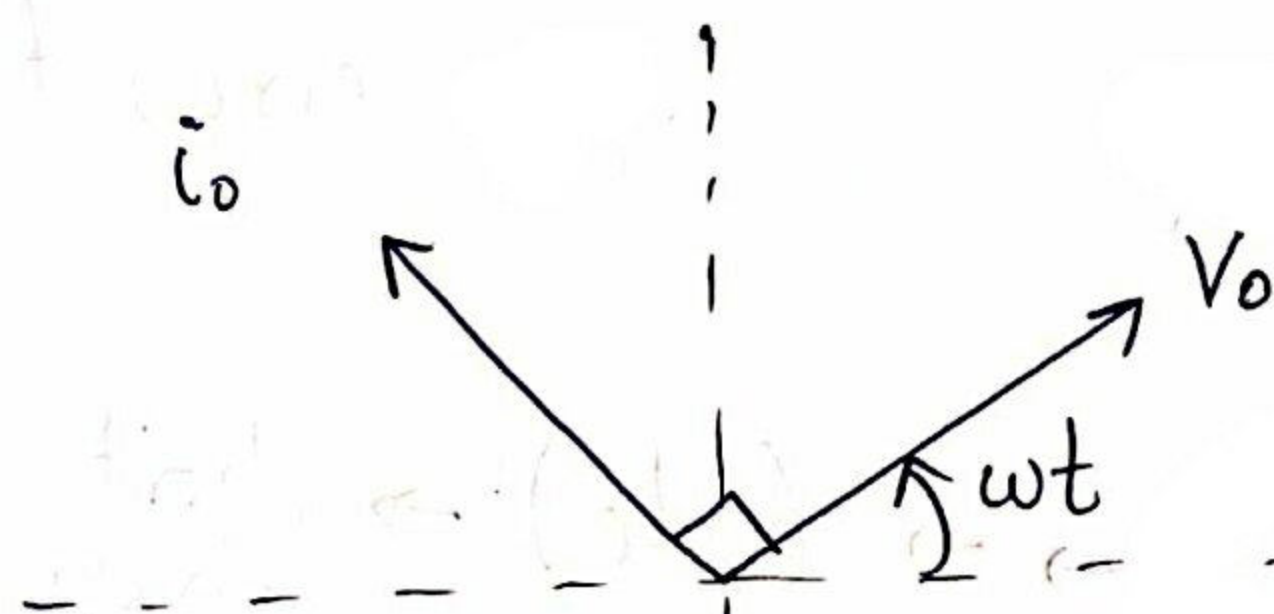current is ahead of voltage by phase of $\pi/2$




$$\begin{cases} V \rightarrow 0 \\ i \rightarrow i_0 \end{cases}$$

independent on phase.

$$V_0 = X_C i_0$$

relation between amplitudes

Inductive load

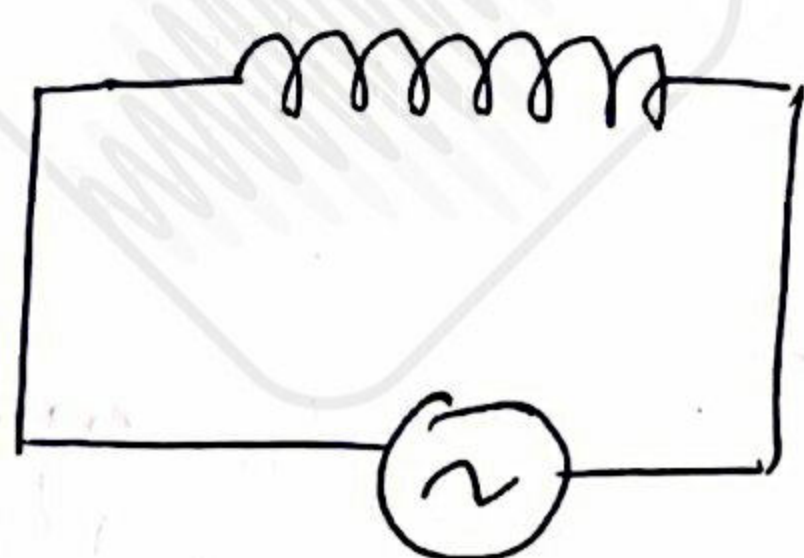

$$V_L(t) = V_0 \sin \omega t$$

$$V_L(t) = V_0(t)$$

$$V_L(t) = V_0 \sin \omega t$$

$$\text{as, } V_L(t) = L \frac{di_L}{dt}$$

$$\Rightarrow i_L = \int \frac{V_L(t)}{L} dt$$

$$\Rightarrow i_L = \frac{1}{L} \int V_0 \sin \omega t dt$$

$$i_L = -\frac{V_0}{\omega L} (\cos \omega t)$$

$$i_L(t) = \frac{V_L}{\omega L} (-\cos \omega t)$$

$\omega L = X_L \cdot \text{unit} \rightarrow (\text{ohm})$

 $X_L \rightarrow \text{inductance reactance}$

 $\omega L \rightarrow \text{Inductive reactance}$

$\Rightarrow \omega \rightarrow \infty, X_L \rightarrow \infty \rightarrow i_L(t) \rightarrow 0$ open circuit.


 $\Rightarrow \omega \rightarrow 0, X_L \rightarrow 0 \rightarrow i_L(t) \rightarrow \infty$ (dc) $\rightarrow$ short circuit

$$\Rightarrow i_L(t) = \frac{V_L}{X_L} \left[\sin(\omega t - \pi/2) \right] = \frac{V_L}{X_L} (-\cos \omega t)$$


as

$\Rightarrow$ Current is behind voltage by $\pi/2$ phase.

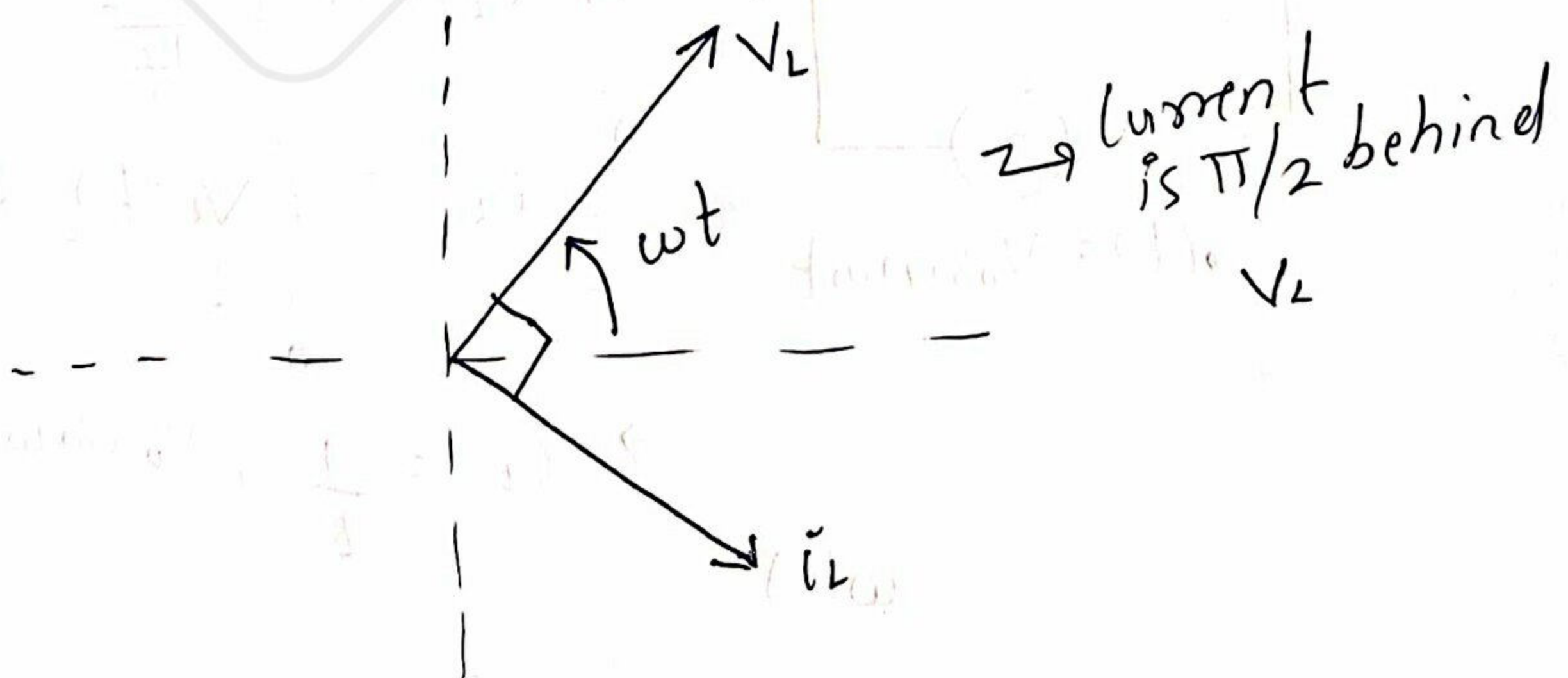through $\left[i_0 = \frac{V_0}{X_L} \right] \rightarrow$ no relation to phase



Series R-L

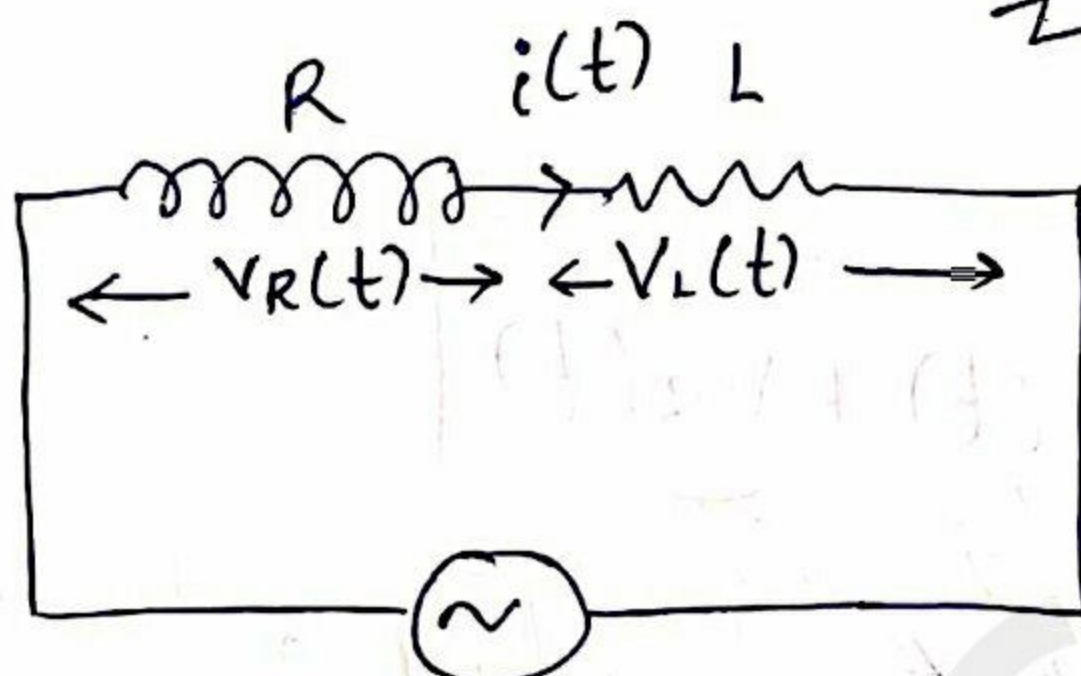

$$v(t) = V_0 \sin(\omega t)$$


in series, so current in each element will be same at any instant.

Now at any instant

$$V(t) = V_R(t) + V_L(t)$$

↳ Kirchhoff's rule.

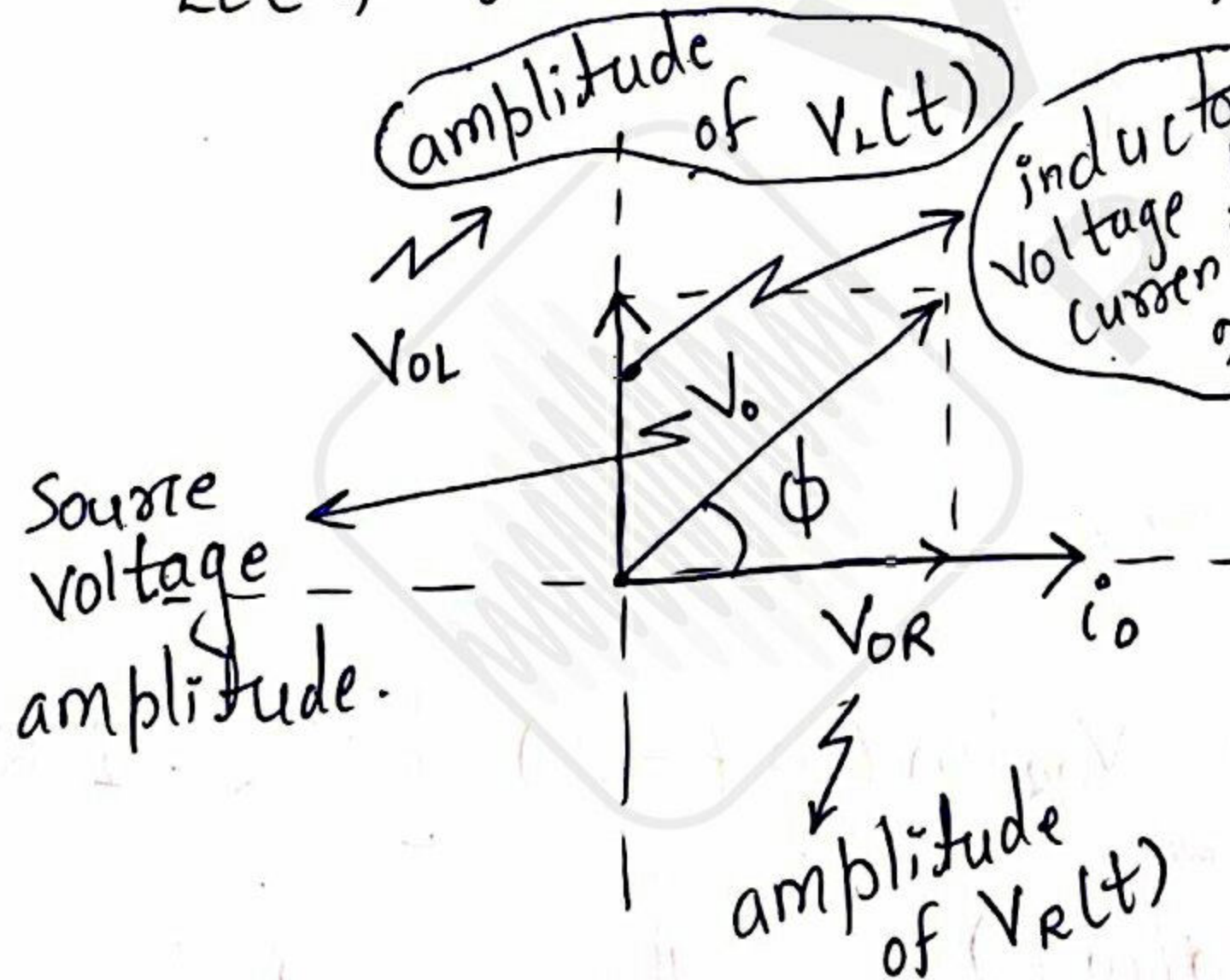Let, $i(t) = \hat{i}_0 \sin(\omega t - \phi)$



now, as, $V_0^2 = V_{0R}^2 + V_{0L}^2$

as $V_{0R} = R \hat{i}_0$

& $V_{0L} = X_L \hat{i}_0$

So,

$$V_0 = \hat{i}_0 \sqrt{R^2 + X_L^2}$$

So, $\frac{V_0}{\hat{i}_0} = \sqrt{R^2 + X_L^2}$

Impedance of circuit

↳ Total resistance is stan

$$Z = \sqrt{R^2 + X_L^2} = \text{Impedance}$$

$$X_L \rightarrow \Omega, R \rightarrow \Omega$$

but $Z \neq R + X_L$ they add up with their phase.

Now $\tan \phi = \frac{V_L}{V_R} = \frac{X_L}{R}$


phase diff between V & I

★ for RL circuit voltage leads current by some phase.

★ $V_0 \neq V_L + V_R$

But,

$$V(t) = V_L(t) + V_R(t)$$

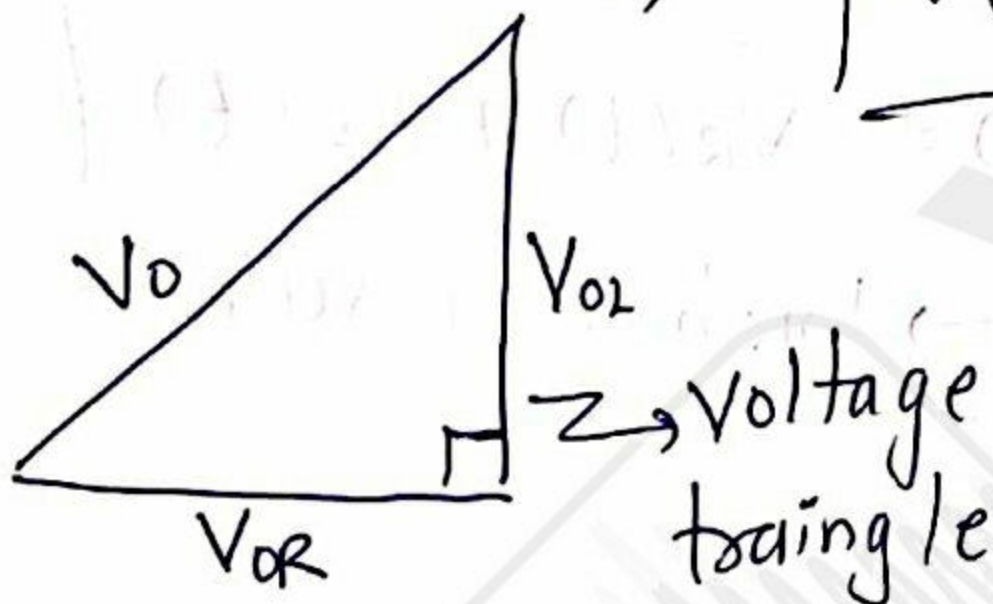

Instantaneous values get add up to give value of instant source voltage

for exact mathematical derivation

$$v(t) = V_0 \sin(\omega t)$$

$$i(t) = i_0 \sin(\omega t - \phi)$$

as, $V_R(t) = i(t) R = V_{0R} \sin(\omega t - \phi)$ [$V_{0R} = i_0 R$]

As we know

$$V_L(t) = V_{0L} \sin(\omega t)$$

$$i_L(t) = i_{0L} \sin(\omega t - \pi/2)$$

current lags by 90°

Now, we can also say

$$V_L(t) = V_{0L} \sin(\omega t - \phi + \pi/2) \quad \text{if } i_L(t) = i_0 \sin(\omega t - \phi)$$

V_L leads by 90°

as, we know $\sin(\pi/2 + \omega t - \phi) = \cos(\omega t - \phi)$

So, $V_L(t) = V_{0L} \cos(\omega t - \phi)$

also, $V_{0L} = i_0 X_L$

As $V_R(t) = V_R(t) + V_L(t)$

$$V_0 \sin \omega t = V_{0R} \sin(\omega t - \phi) + V_{0L} \cos(\omega t - \phi) \quad \text{--- (i)}$$

→ This will always be valid.

so if $t = t + T/4$, still valid

So, $\omega(T/4) = \pi/2 = \text{phase.}$

$$\Rightarrow V_0 \sin(\omega t + \pi/2) = V_{0R} \sin(\omega t - \phi + \pi/2) + V_{0L} \cos(\omega t - \phi + \pi/2)$$

so or $V_0 \cos(\omega t) = V_{0R} \cos(\omega t - \phi) + [-V_{0L} \sin(\omega t - \phi)]$

$$V_0 \cos(\omega t) = V_{0R} \cos(\omega t - \phi) - V_{0L} \sin(\omega t - \phi) \quad \text{--- (ii)}$$


now $(i)^2 + (ii)^2$

We will get:

$$\boxed{V_0^2 = V_{0R}^2 + V_{0L}^2} \rightarrow \text{Same as per phasor analysis.}$$

Same result!

Series R-C circuit:

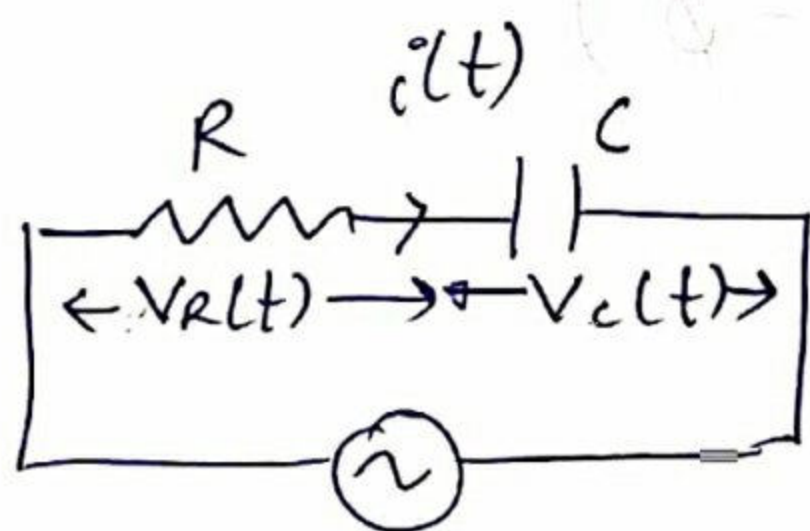

$$V(t) = V_0 \sin \omega t$$

$$V(t) = V_0 \sin \omega t$$


$$\& \boxed{V(t) = V_R(t) + V_C(t)}$$

← Kirchhoff's law

$$V_{0R} = i_0 R$$

$$V_{0C} = i_0 X_C$$

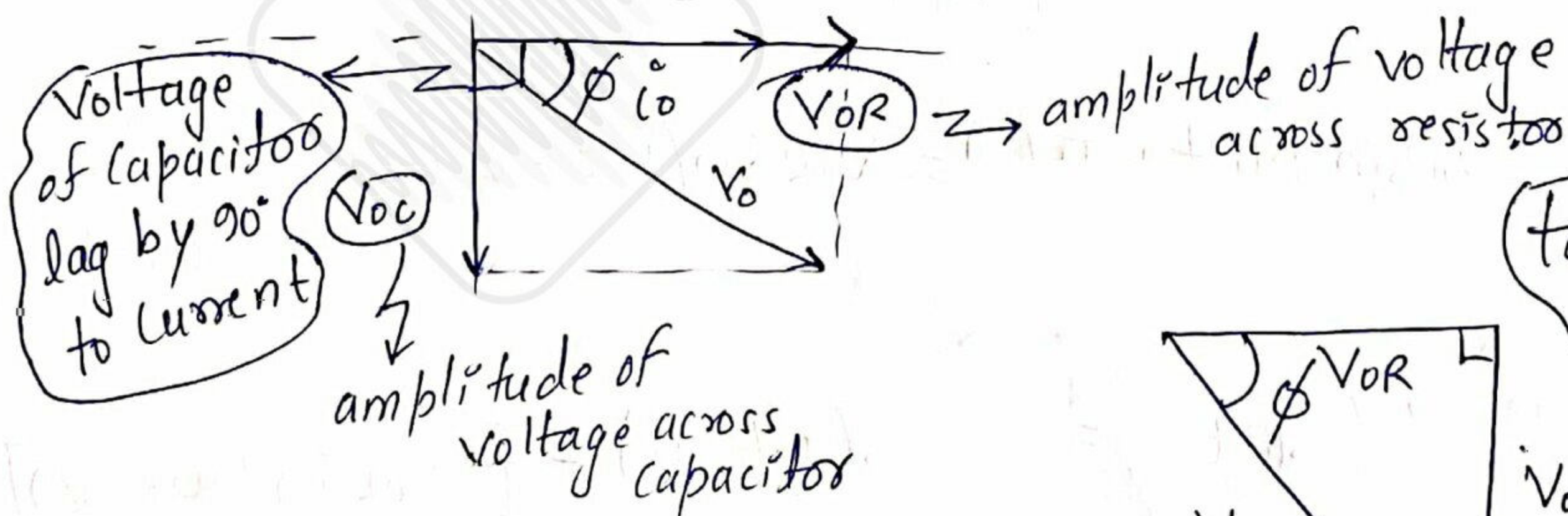for resistor current and voltage are in phase.




$$\tan \phi = \frac{V_{0C}}{V_{0R}} = \frac{X_C}{R}$$

Now here again

$$\text{Impedance } \Rightarrow \boxed{Z = \sqrt{R^2 + X_C^2}}$$

Voltage triangle

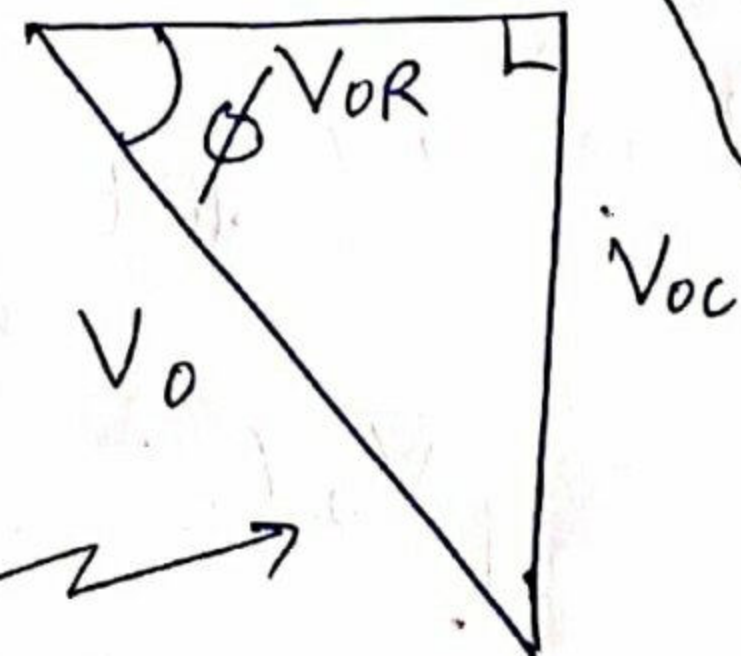


And from voltage triangle

$$V_0^2 = V_{or}^2 + V_{oc}^2$$

but $V_0 \neq V_{or} + V_{oc}$, $V_0(t) = V_R(t) + V_C(t)$

Series LC Circuit:

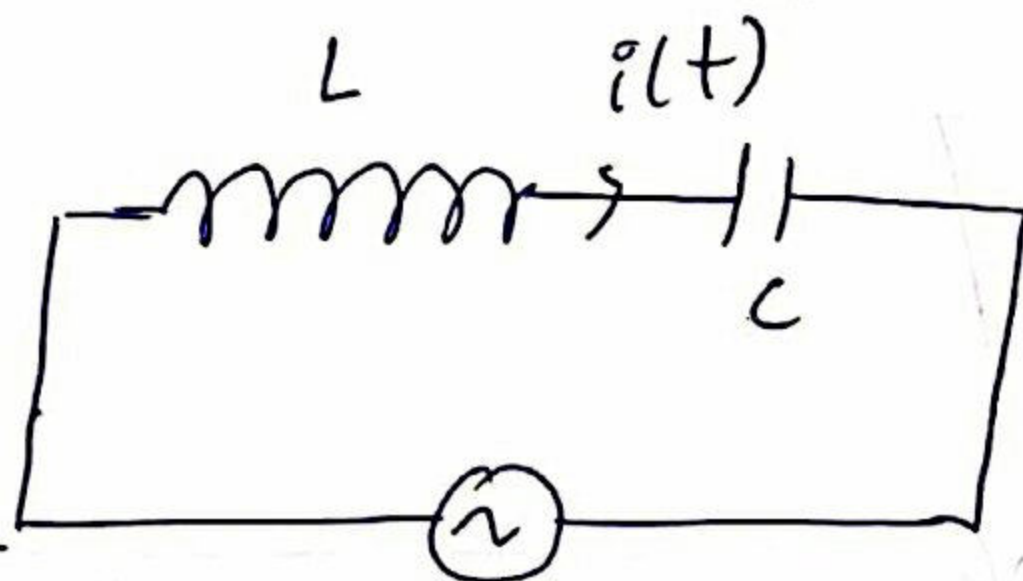

$$V(t) = V_0 \sin(\omega t)$$


$$V_0(t) = V_L(t) + V_C(t)$$

Kirchhoff's law


$$\Rightarrow V_0 = V_{OL} - V_{OC} \quad \text{for } V_{OL} > V_{OC}$$

$$\& V_0 = V_{OC} - V_{OL} \quad \text{for } V_{OC} > V_{OL}$$

So,

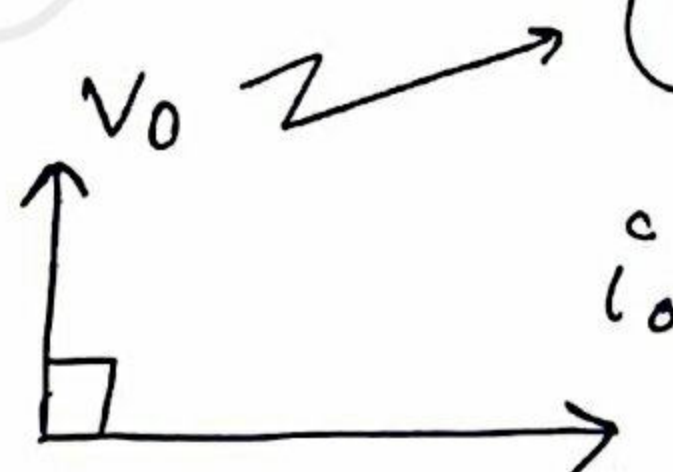

So, $Z = X_L - X_C$ or $X_C - X_L$ depending
or $|Z| = |X_L - X_C|$

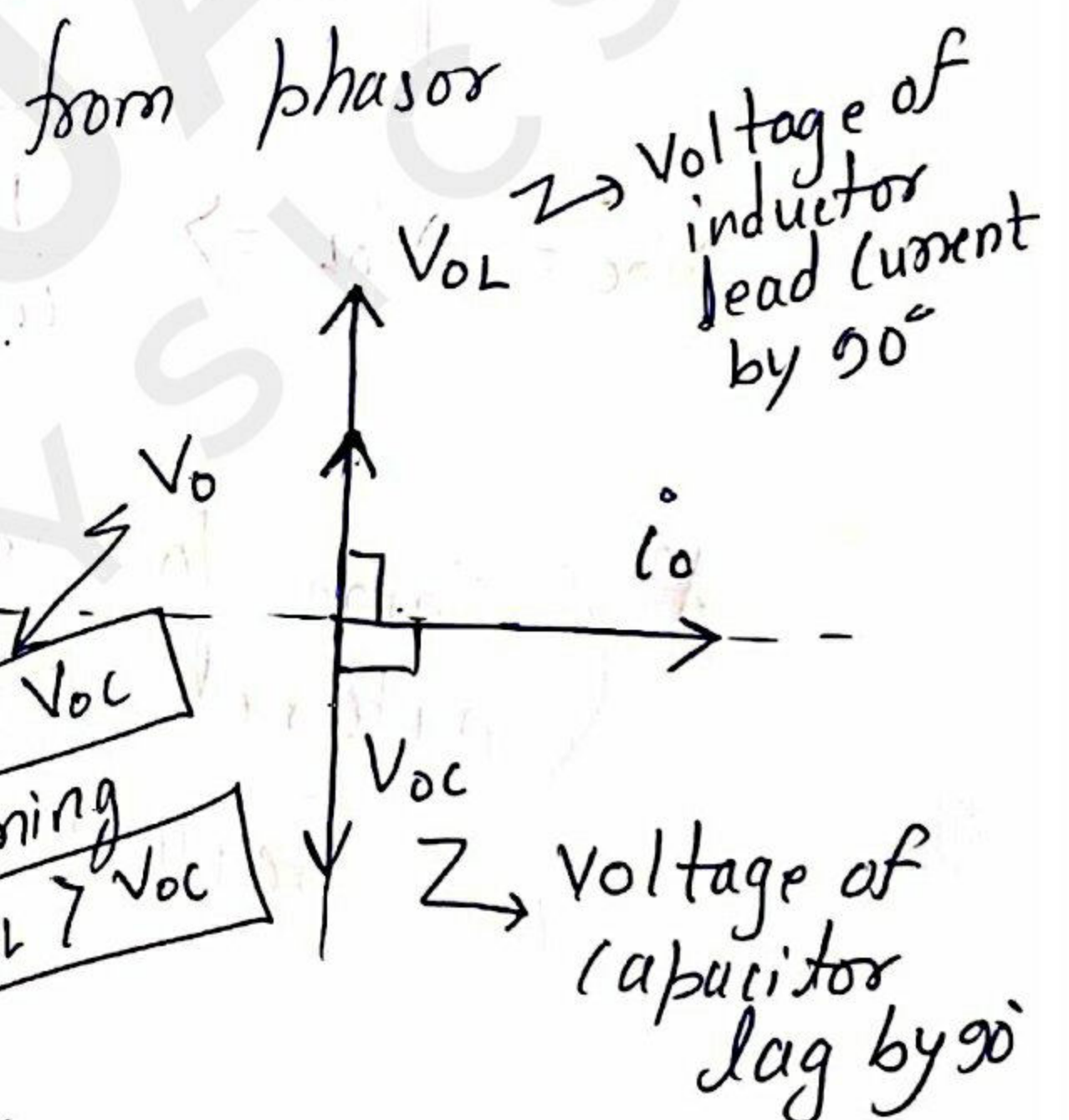

net voltage still lead or lag by 90° from current depending on which is greater V_{or} or V_{oc}

it is possible that:

$$V_{OL} > V_O \text{ \& } V_{OC} > V_O$$

so if $V_{OL} > V_{OC}$ (circuit is more inductive)
if $V_{OC} > V_{OL}$ (circuit is more capacitive)

if $V_{OC} = V_{OL}$
then $Z = 0$, so current $i \rightarrow \infty$

as,
$$i_0 = \frac{V_O}{Z}$$

$$V_{OC} = V_{OL} \Rightarrow \frac{1}{\omega C} = \omega L$$


or

$$\omega = \sqrt{\frac{1}{LC}} = \omega_0$$

* Same to be natural angular frequency of LC circuit

so if outside frequency ω , reach ω_0 circuit is in resonance

parallel R-L circuit

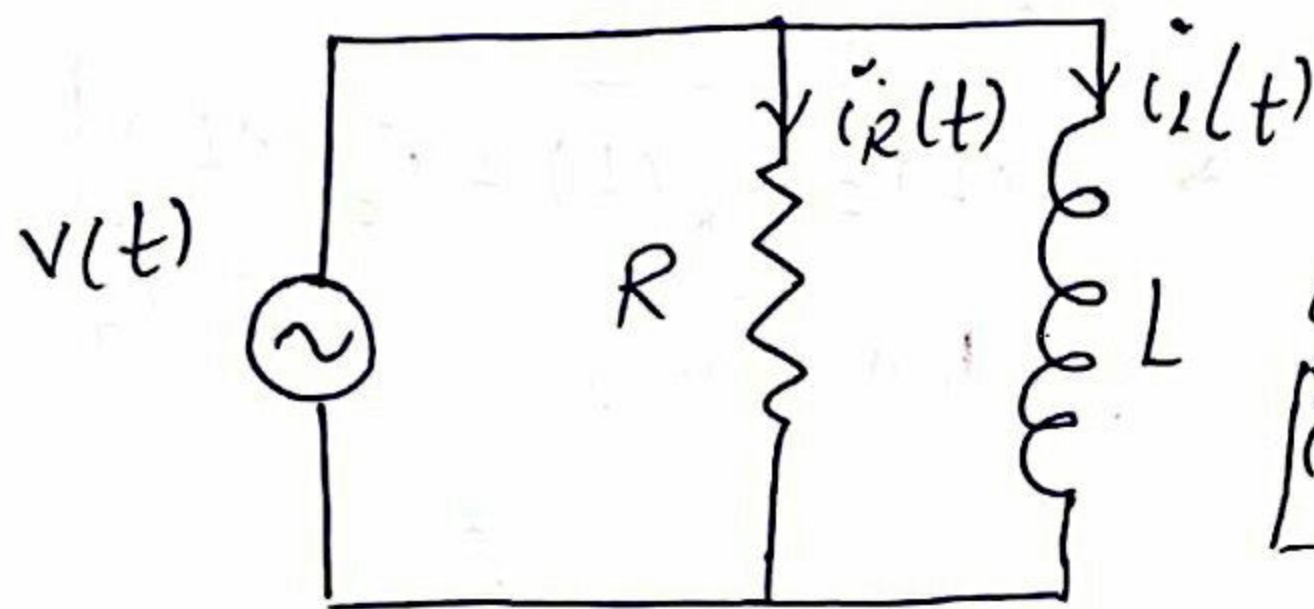


$$v(t) = V_0 \sin \omega t$$

$$V_R(t) = V_0 \sin \omega t = V_L(t)$$

$$i_{0R} = \frac{V_0}{R} = \frac{V_{0R}}{R}$$

$$i_{0L} = \frac{V_0}{X_L} = \frac{V_{0L}}{X_L}$$
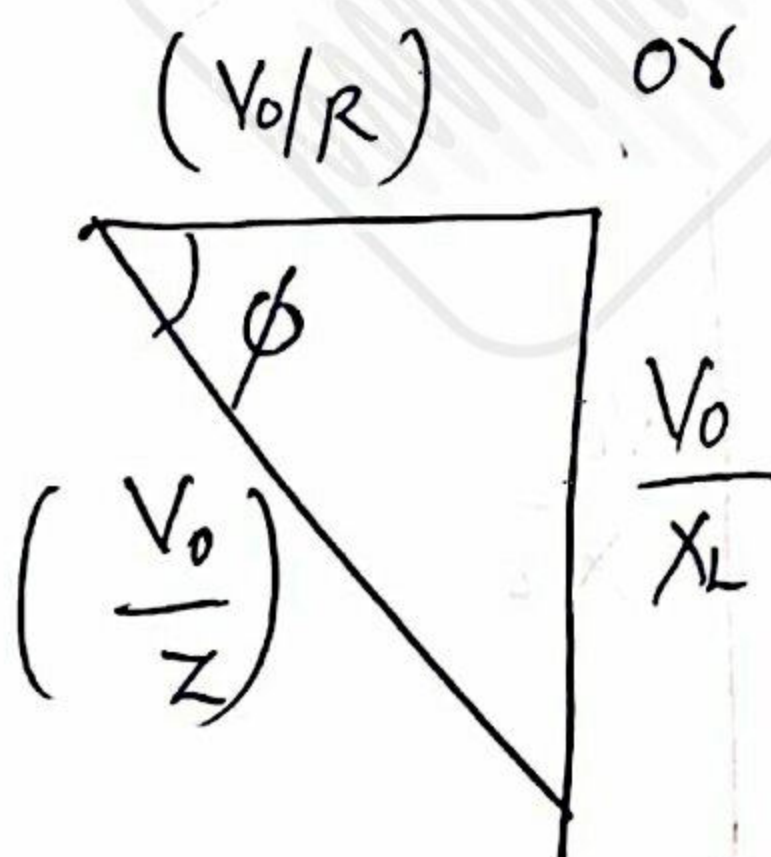
$$i_0^2 = \sqrt{(i_{0R})^2 + (i_{0L})^2}$$





As elements are in parallel voltages amplitude across the elements will be same


at any instant:

$$i(t) = i_R(t) + i_L(t)$$

Kirchhoff's law

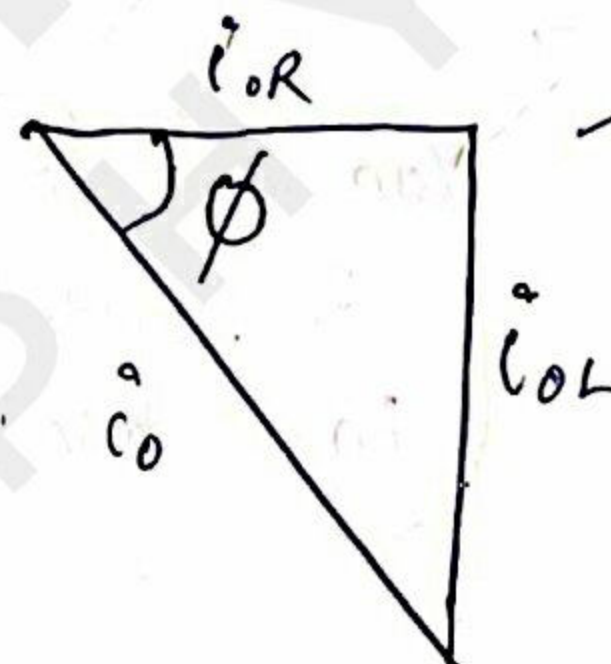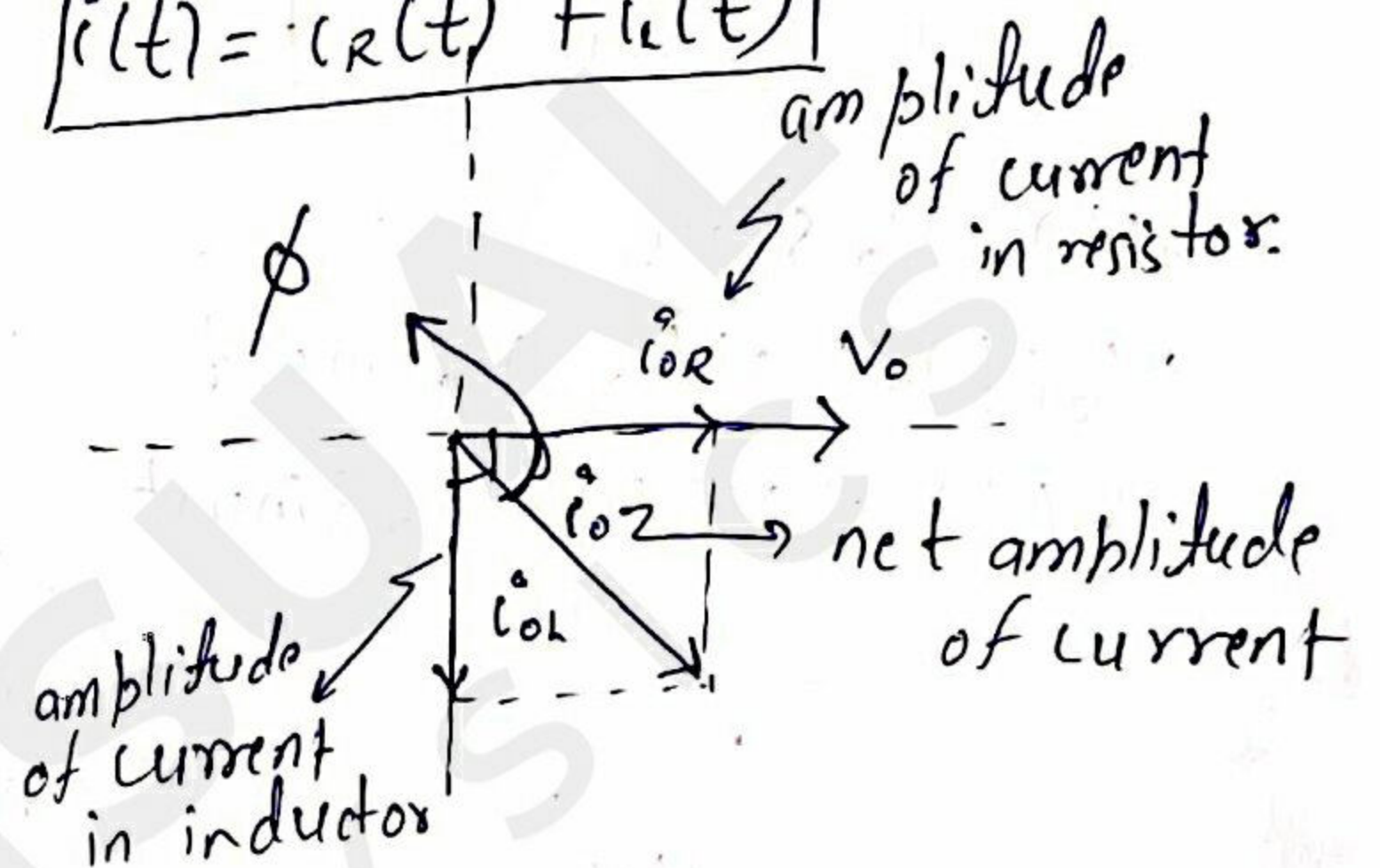


Current triangle

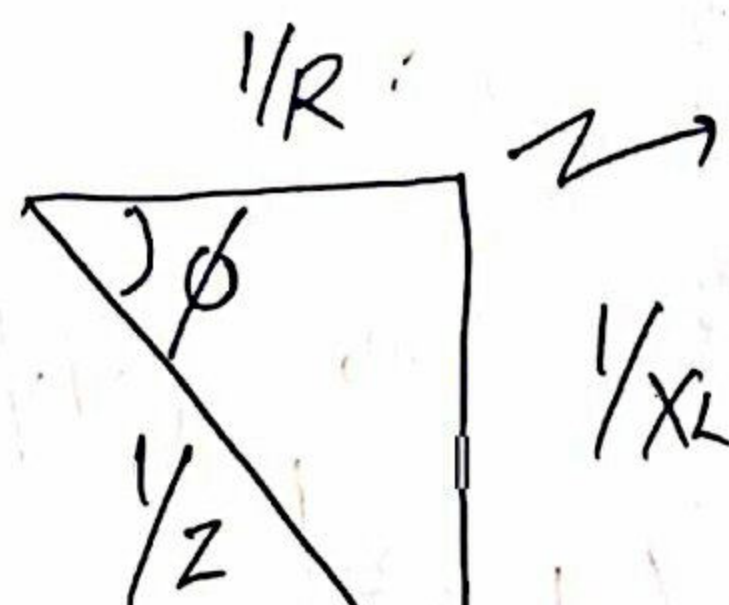

inverse impedance triangle

$$\left| \left(\frac{1}{Z} \right)^2 = \left(\frac{1}{R} \right)^2 + \left(\frac{1}{X_L} \right)^2 \right|$$

parallel R-C circuit :

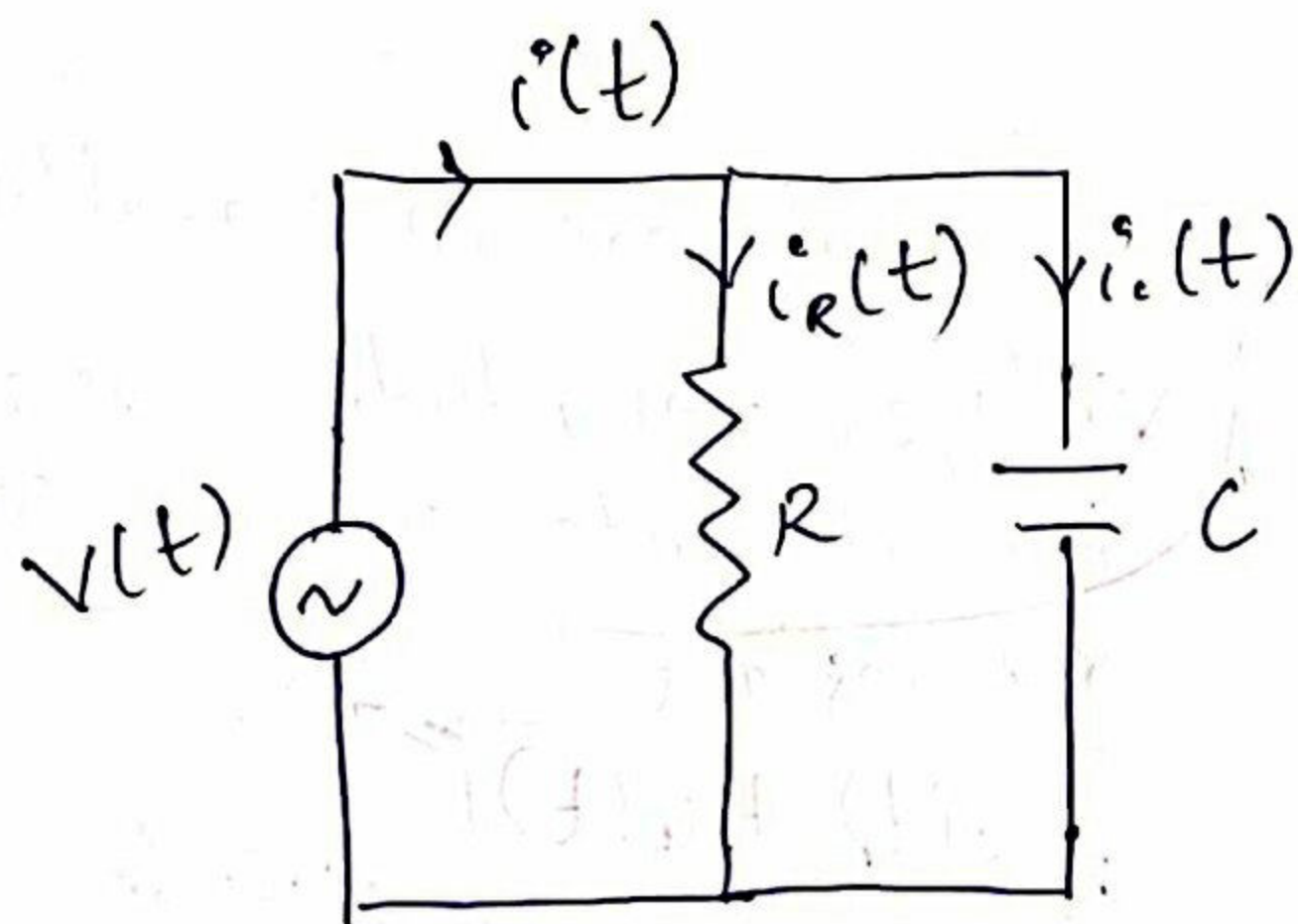

Similarly as discussed for parallel R-L circuit:


$$\Rightarrow \boxed{i(t) = i_R(t) + i_C(t)}$$

Kirchhoff's junction law

$$V(t) = V_0 \sin \omega t$$

$$V_R(t) = V(t) = V_0 \sin \omega t$$

$$V_C(t) = V(t) = V_0 \sin \omega t$$

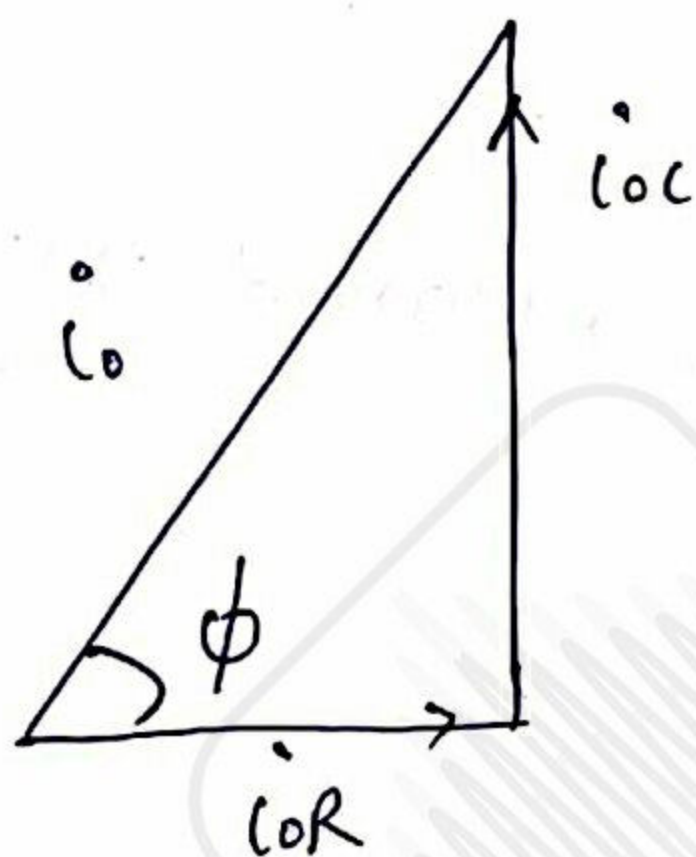

as lead current by 90° to voltage

amplitude of current in capacitor


amplitude of current in resistor.

$$i_{0C} = \frac{V_0}{X_C}$$


$$i_{0R} = \frac{V_0}{R}$$

$$\boxed{\left(\frac{1}{Z}\right)^2 = \left(\frac{1}{X_C}\right)^2 + \left(\frac{1}{R}\right)^2}$$

So,

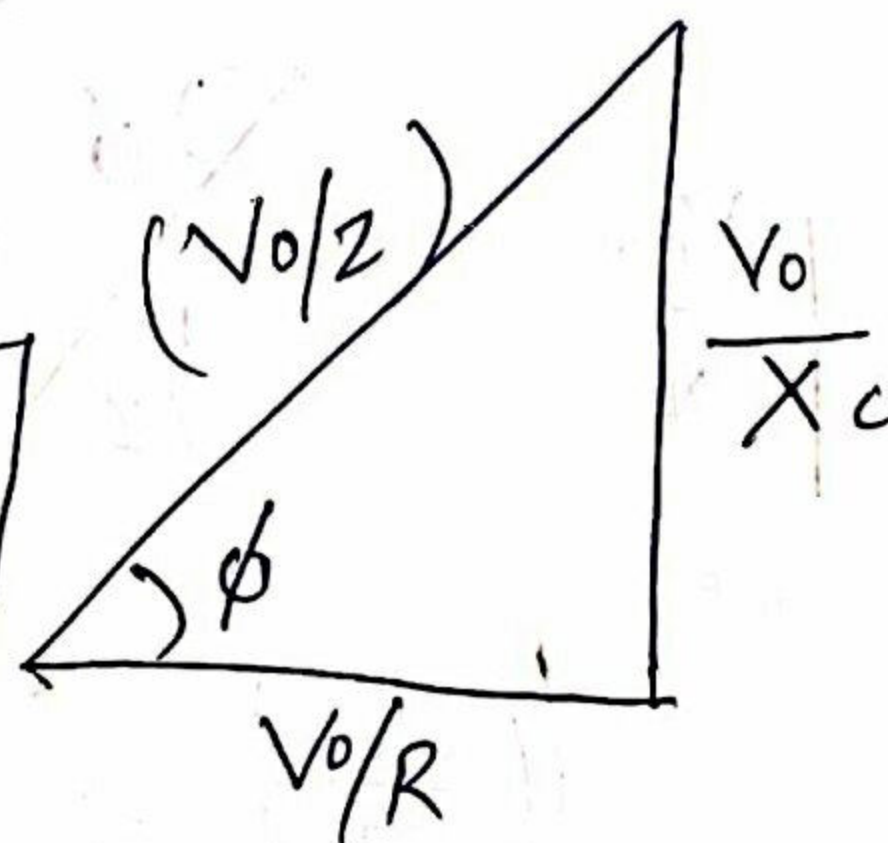

parallel C-L circuit:

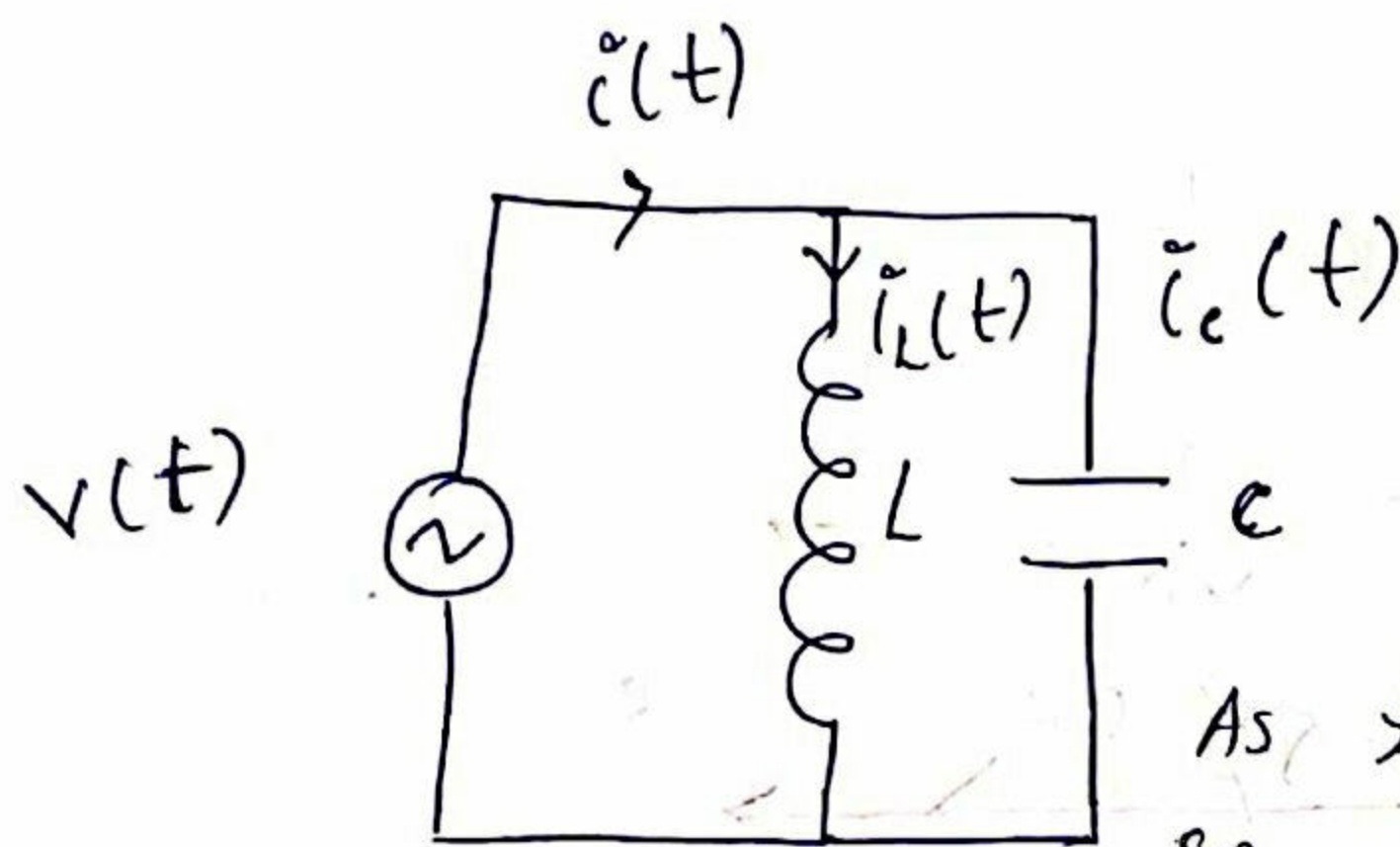

at any instant

$$\boxed{i(t) = i_L(t) + i_C(t)}$$

↓ Kirchhoff's junction law:
As the elements are in parallel:

so, $V(t) = V_L(t) = V_C(t)$


$$V(t) = V_0 \sin \omega t = V_L(t) = V_C(t)$$

$$i_{0L} = \frac{V_0}{X_L}, \quad i_{0C} = \frac{V_0}{X_C}$$


Net amplitude of current

$$i_0 = i_{0C} - i_{0L} \quad [\text{if } i_{0C} > i_{0L}]$$

$$\boxed{Z = X_C - X_L}$$

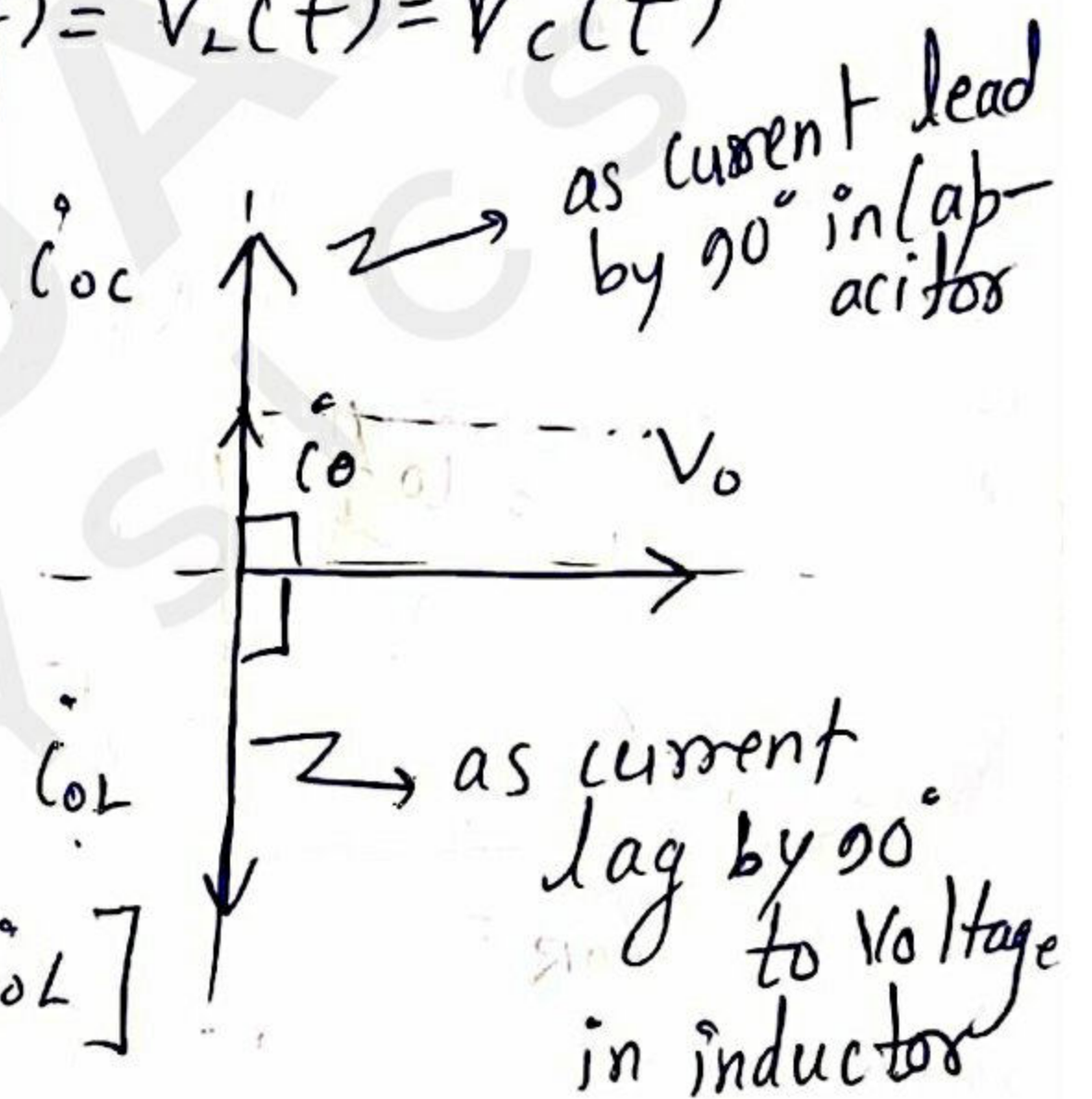

Series R-L-C circuit:


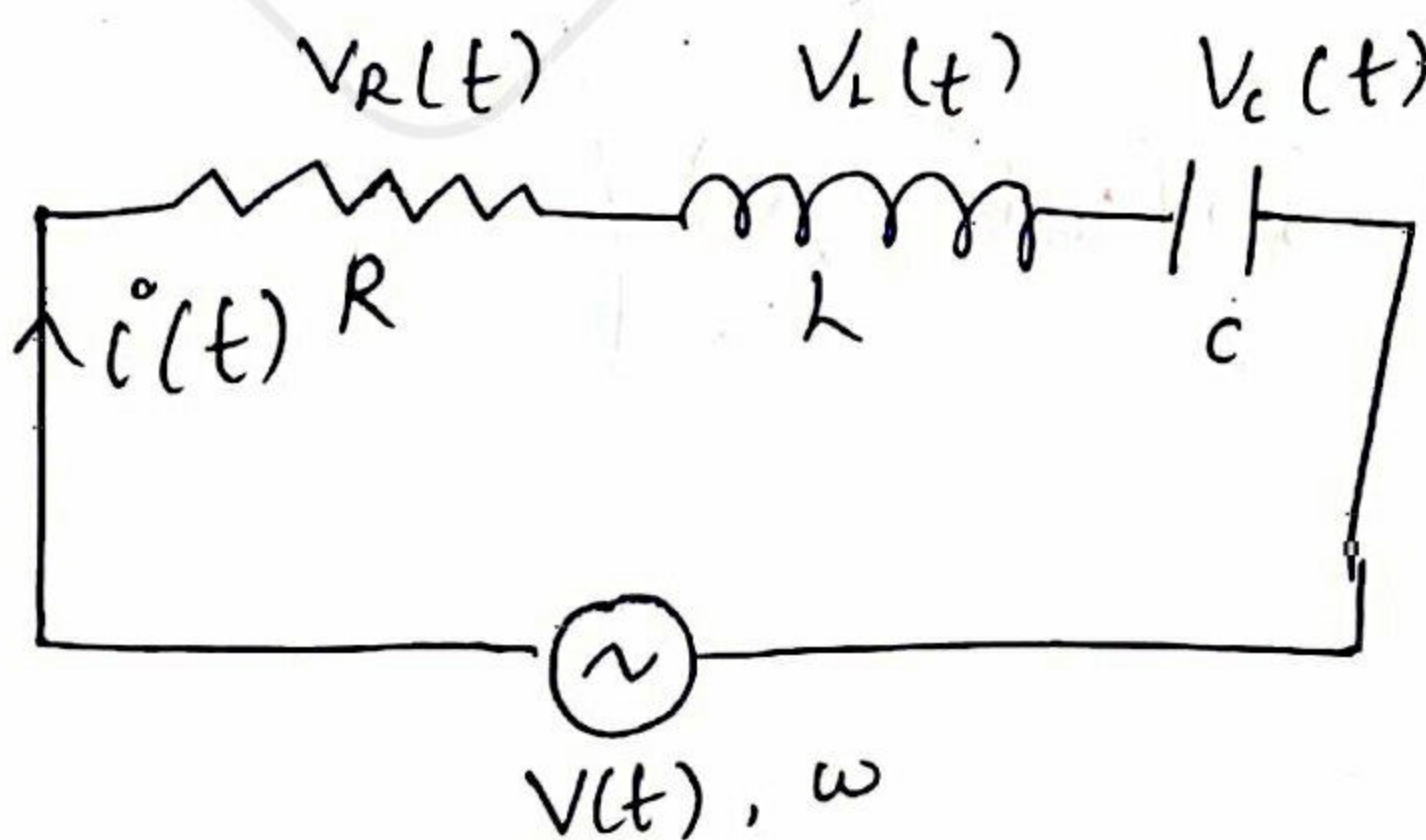


So,

$$V(t) = V_R(t) + V_L(t) + V_C(t)$$

$$V(t) = V_0 \sin \omega t$$
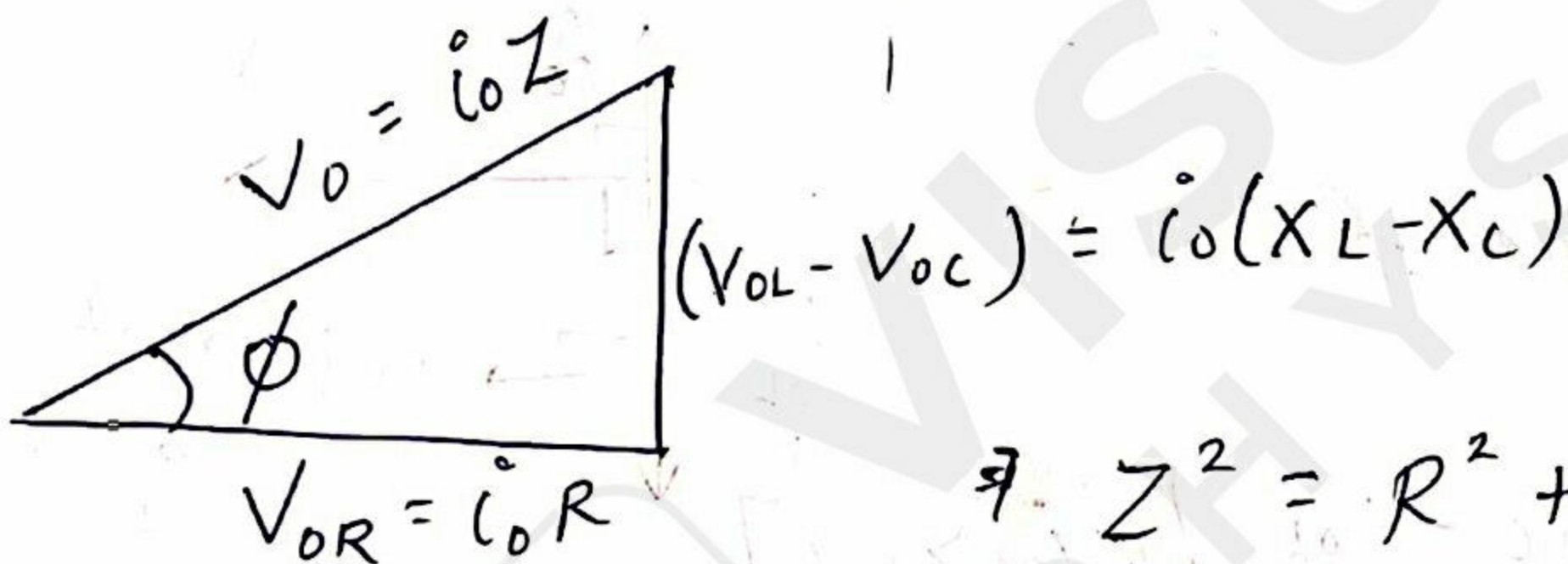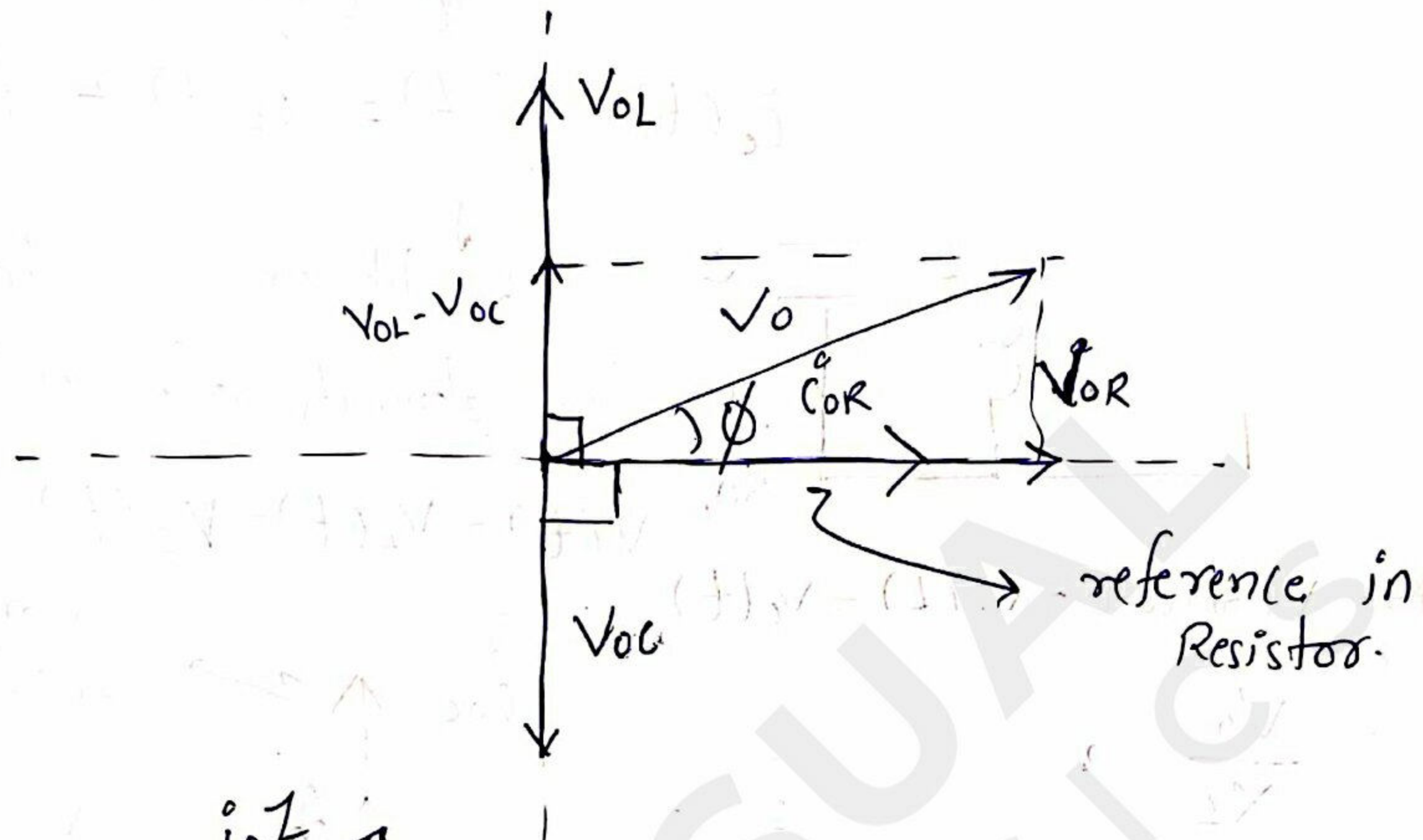
$$\dot{I}_{OR} = \frac{V_{OR}}{R}, \quad \dot{I}_{OL} = \frac{V_{OL}}{X_L}, \quad \dot{I}_{OC} = \frac{V_{OC}}{X_C}$$



$$Z^2 = R^2 + (X_L - X_C)^2$$


$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$\left(\dot{I}_0 = \frac{V_0}{Z} \right)$$

$$\tan \phi = \frac{(X_L - X_C)}{R}$$

$$\text{So, } \boxed{\dot{i} = \dot{I}_0 \sin(\omega t - \phi)}$$

Parallel RLC circuit

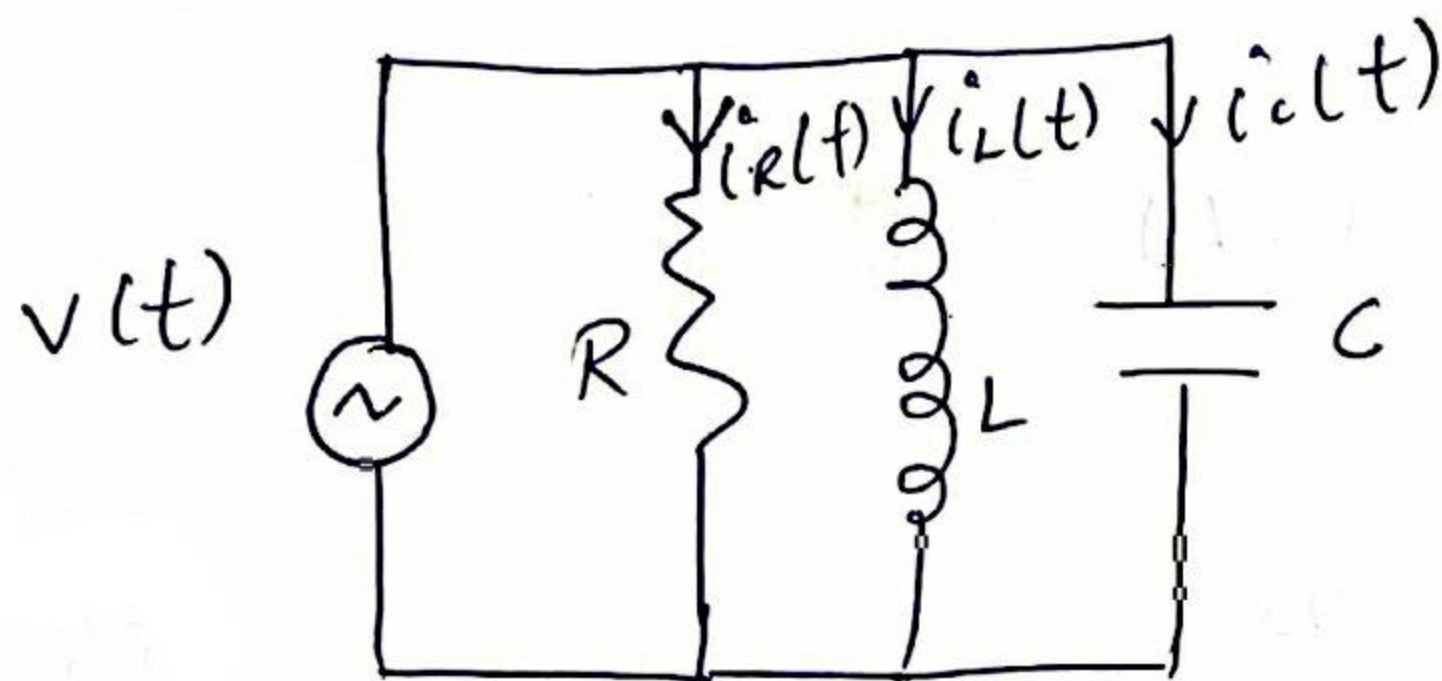


$$V(t) = V_R(t) = V_L(t) = V_C(t)$$

$$i_o(t) = i_R(t) + i_L(t) + i_C(t)$$


→ Kirchhoff's junction law

$$i_{oR} = \frac{V_o}{R}, \quad i_{oL} = \frac{V_o}{X_L}, \quad i_{oC} = \frac{V_o}{X_C}$$
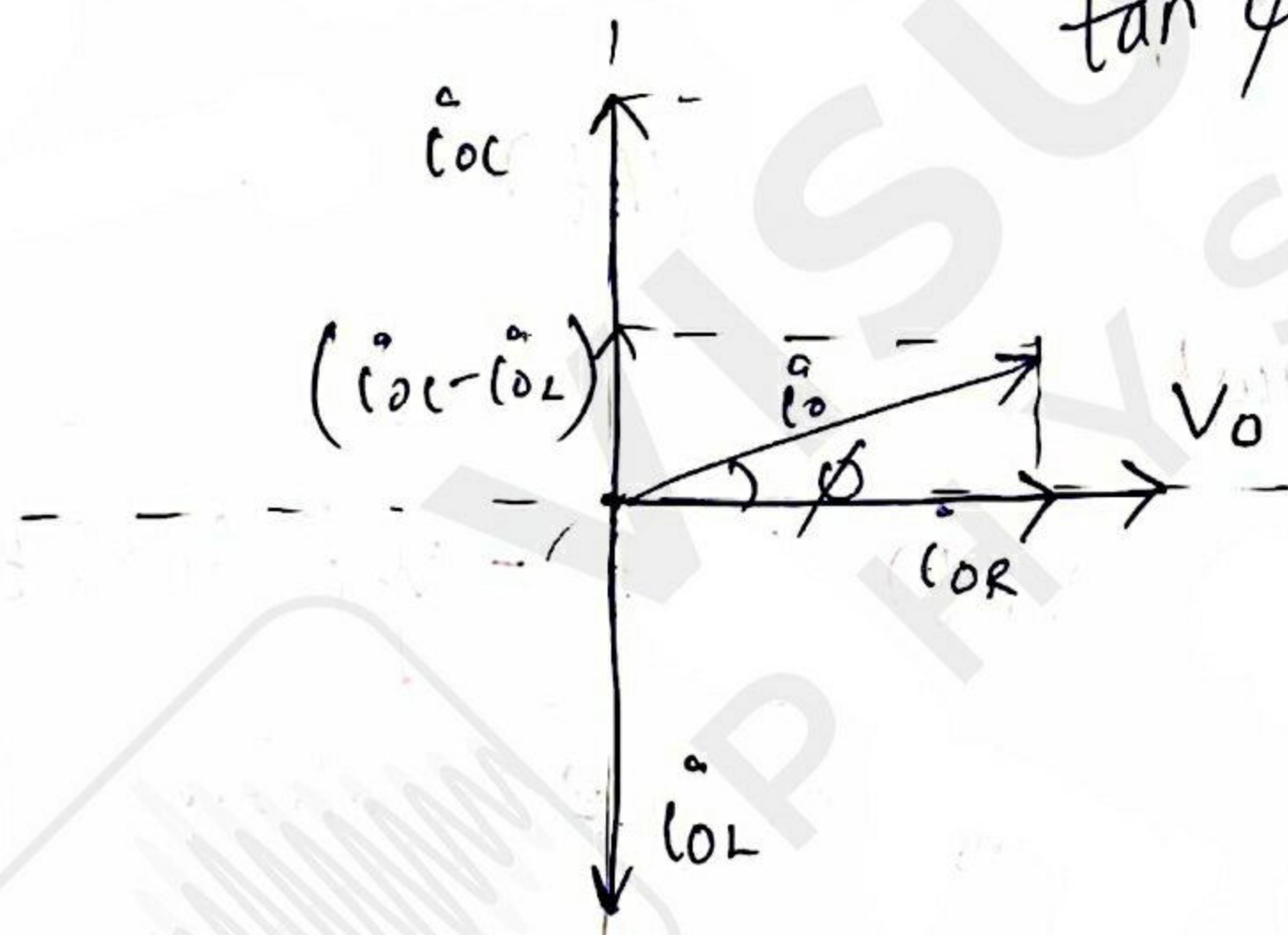
$$\tan \phi = \frac{(i_{oC} - i_{oL})}{i_{oR}}$$


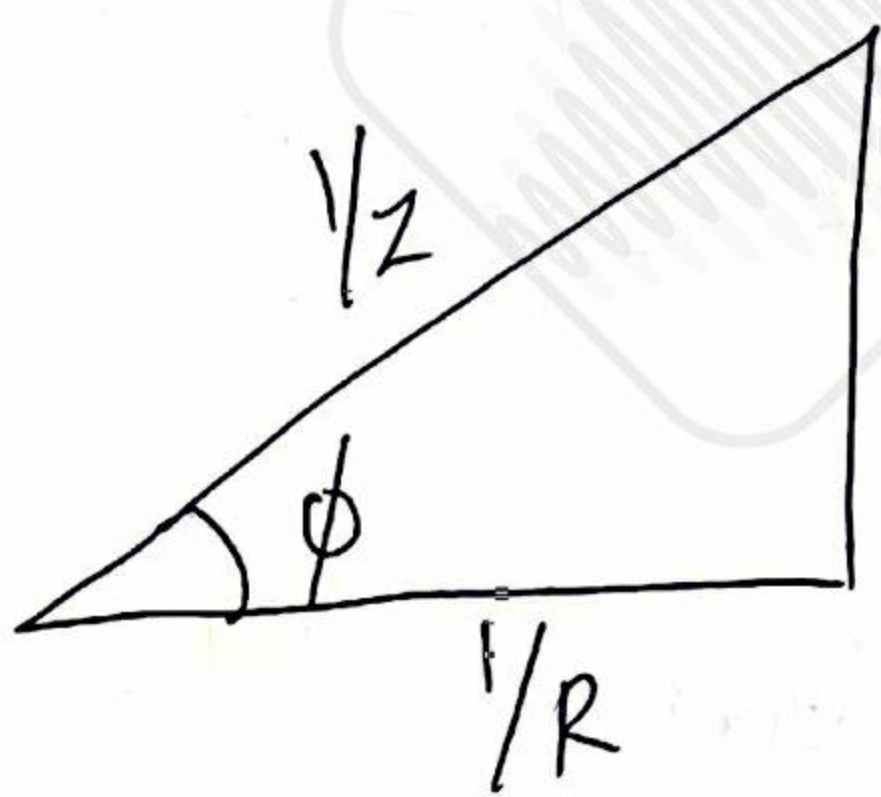
$$\tan \phi = \frac{\frac{1}{X_C} - \frac{1}{X_L}}{\frac{1}{R}}$$



$$\left(\frac{1}{X_C} - \frac{1}{X_L} \right)$$

inverse impedance triangle!


$$\left(\frac{1}{Z} \right)^2 = \left(\frac{1}{R} \right)^2 + \left(\frac{1}{X_C} - \frac{1}{X_L} \right)^2$$

Power

Power supplied by source at any instant:

$$P(t) = V(t) i(t)$$

for Inductor:

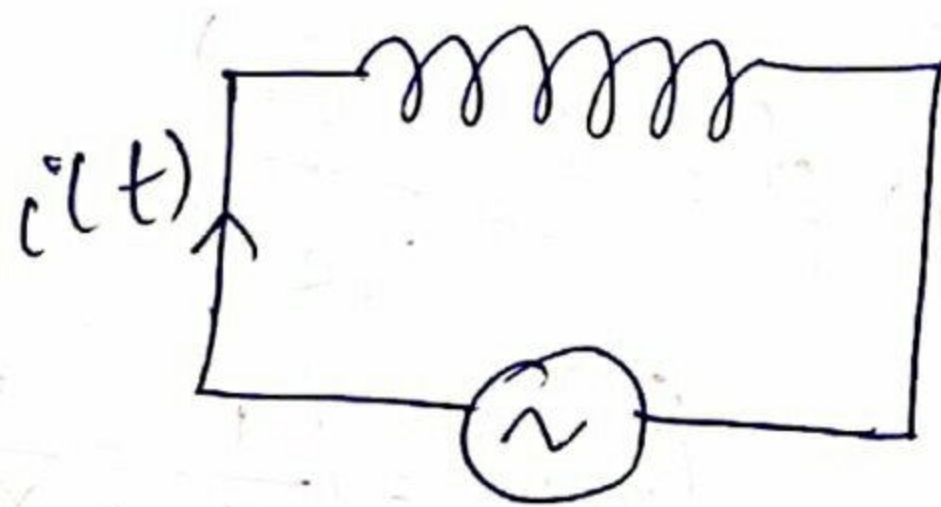

$$V(t) = V_0 \sin \omega t$$

$$i(t) = i_0 \sin(\omega t - \pi/2)$$

$$\text{or } i(t) = -i_0 \cos \omega t$$


$\pi/2$ phase lag to $V(t)$

$$\text{so, } P(t) = V(t) i(t) = -V_0 i_0 \sin \omega t \cos \omega t$$

for average power lost in one complete cycle:

$$\langle P(t) \rangle = - \int_0^T V_0 i_0 \sin \omega t \cos \omega t dt = 0$$

(integration gives)

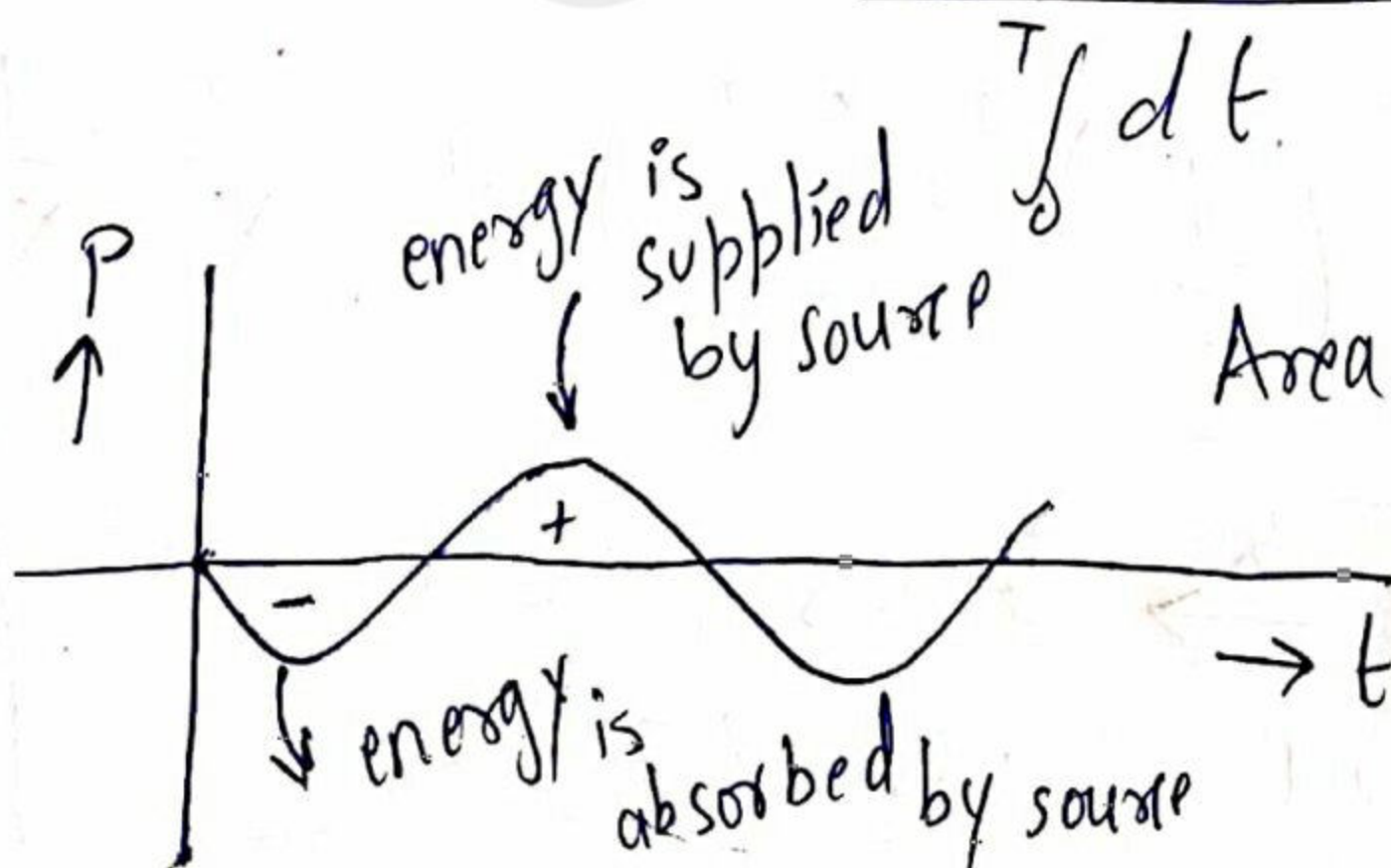


Area under power time graph gives value.

So power lost by pure Inductor in 1 time period is zero.

(90° phase lead)

for capacitor:

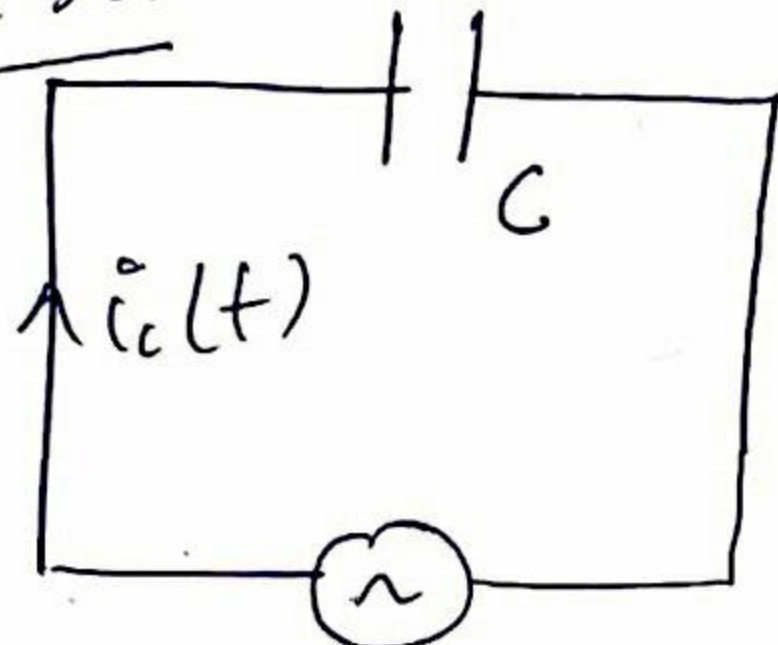

$$V(t) = V_0 \sin \omega t$$

$$\begin{aligned} \tilde{i}_c(t) &= \tilde{i}_0 \sin(\pi/2 + \omega t) \\ &= \tilde{i}_0 \cos \omega t \end{aligned}$$

so instantaneous power lost $P(t) = V_0 \sin \omega t \tilde{i}_0 \cos \omega t$

$$\text{so, } \langle P(t) \rangle = \frac{\int_0^T \tilde{i}_0 V_0 \sin \omega t \cos \omega t dt}{\int_0^T dt}$$

$$\text{as, } \int_0^T \sin \omega t \cos \omega t dt = 0$$


$$\text{so, } \langle P(t) \rangle = 0$$

So similar for the case of inductor, here also power loss in capacitor for one complete cycle is:

$$\langle P(t) \rangle = 0 \rightarrow \text{power lost in one complete cycle}$$

★ In both the element, power given by source get absorb or stored in form of magnetic & Electric field in inductor and capacitor resp.

for resistor:

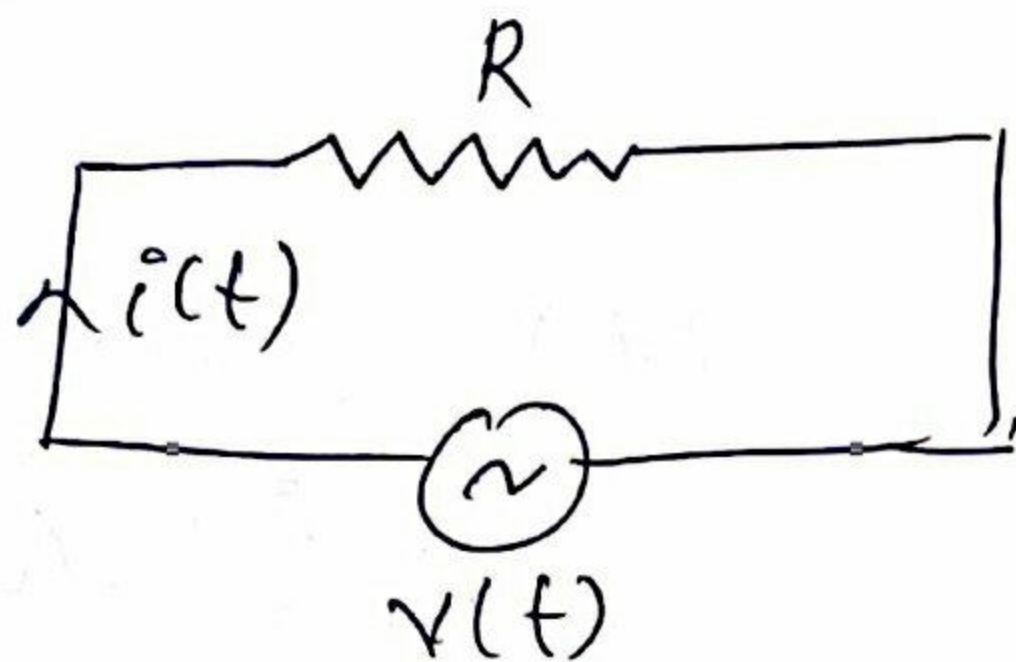

$$V(t) = V_0 \sin \omega t$$

$$i(t) = i_0 \sin \omega t$$

$$P(t) = V(t)i(t) = (V_0 \sin \omega t)(i_0 \sin \omega t)$$

$$P(t) = V_0 i_0 \sin^2 \omega t$$

$$\text{so, } \langle P(t) \rangle = \frac{\int_0^T V_0 i_0 \sin^2 \omega t \, dt}{\int_0^T dt}$$


$$\langle P(t) \rangle = \frac{V_0 i_0 \left(\frac{1}{2} \right) T}{T}$$

$$\text{as, } \int_0^T \sin^2 \omega t \, dt = \left(\frac{1}{2} \right) T$$

$$\boxed{\langle P(t) \rangle = \left(\frac{V_0}{\sqrt{2}} \right) \left(\frac{i_0}{\sqrt{2}} \right) = V_{\text{rms}} i_{\text{rms}}}$$

so, resistor element lost the power in 1 cycle by $V_{\text{rms}} i_{\text{rms}}$

Now power lost in RLC series!

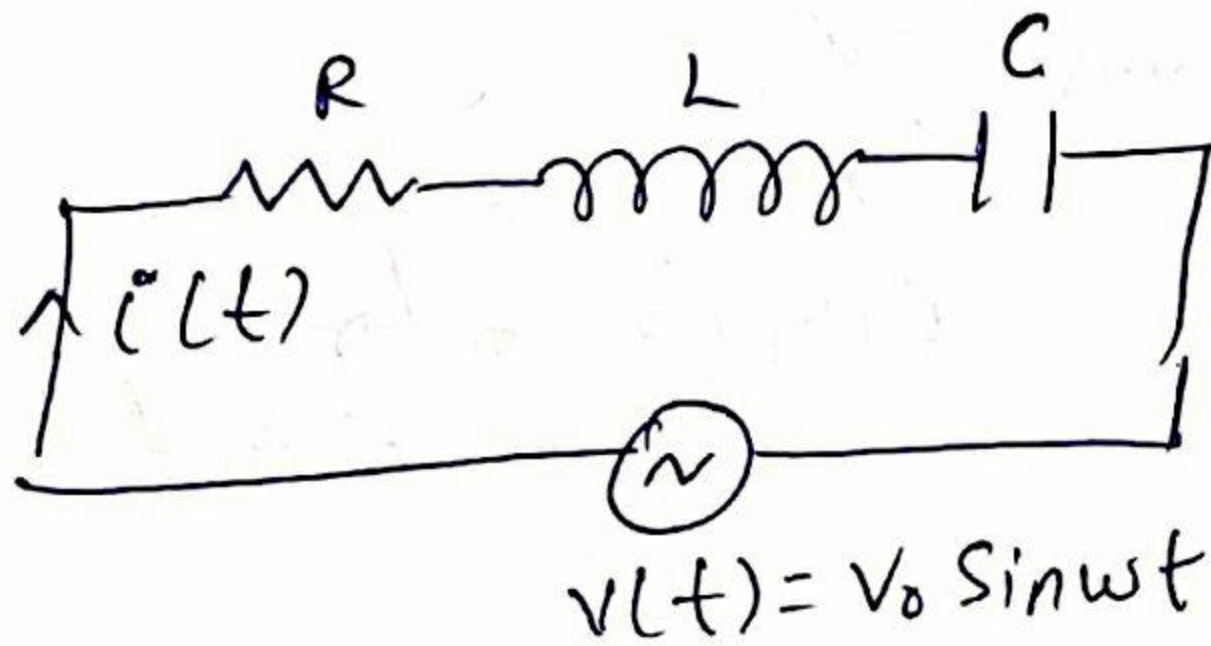

$$\tan \phi = \frac{(X_L - X_C)}{R}$$

so, now $i(t) = i_0 \sin(\omega t - \phi)$

Power lost in any instant

$$P(t) = v(t) i(t) \\ = V_0 \sin \omega t \cdot i_0 \sin(\omega t - \phi)$$

so, $\langle P(t) \rangle = \frac{\int_0^T i_0 V_0 \sin \omega t \sin(\omega t - \phi) dt}{\int_0^T dt}$

(average power lost in 1 cycle)

$$\langle P(t) \rangle_T = i_0 V_0 \int_0^T \sin \omega t [\sin \omega t \cos \phi - \cos \omega t \sin \phi] dt$$

$$= i_0 V_0 \left[\cos \phi \int_0^T \sin^2 \omega t dt - \sin \phi \int_0^T \sin \omega t \cos \omega t dt \right]$$

$$\langle P(t) \rangle_T = \frac{i_0 V_0 \cos \phi}{2} T$$

$\swarrow$ (1/2)
 $\swarrow$ zero

$$\langle P(t) \rangle = \frac{V_0 i_0 \cos \phi}{2}$$

$$\boxed{\langle P(t) \rangle = V_{\text{rms}} i_{\text{rms}} \cos \phi}$$

⚡
Power lost

↙ power factor
of the circuit

$$\text{Also, } \boxed{V_0 \cos \phi = V_R}$$

↘ Voltage drop component across resistor.


Q - factor

for series RLC circuit

$$i_0 = \frac{V_0}{Z} = \frac{V_0}{\sqrt{R^2 + (X_L - X_C)^2}}$$

$$\text{or } \boxed{i_0 = \frac{V_0}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C} \right)^2}}}$$

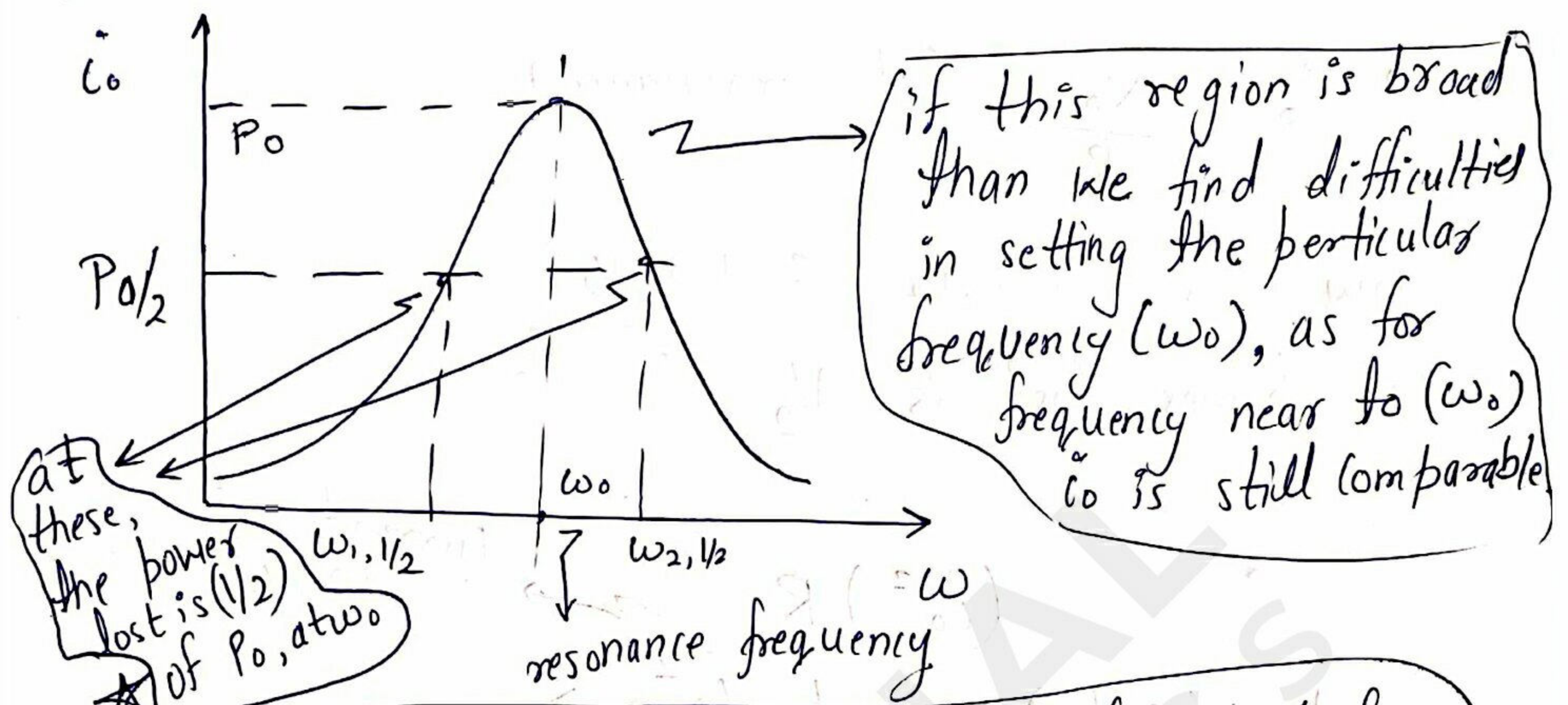So if we plot the variation of current with respect to frequency we get:



For tuning we set the resonance frequency ω_0 for particular signal.

So we need the region to be very sharp, so that we find the signal and set the RLC circuit easily to its resonance frequency.

Sharpness of Resonance curve is measured by Q-factor

$$Q = \frac{\omega_0}{\omega_{2,1/2} - \omega_{1,1/2}}$$

Higher Q, sharper Q

Typically 10:100

at resonance, $X_C = X_L$

$$\tilde{i}_0 = \frac{V_0}{R} \quad (\text{at resonance})$$

$$P_0 = (\tilde{i}_0)^2 R$$

now at $\omega_{1,1/2}$ & $\omega_{2,1/2}$

$\tilde{i}_{1/2}$ is the current

$$\Rightarrow (\tilde{i}_{1/2})^2 R = \frac{1}{2} P_0 = \frac{1}{2} (\tilde{i}_0)^2 R$$

$$\Rightarrow \boxed{\tilde{i}_{1/2} = \frac{\tilde{i}_0}{\sqrt{2}}}$$

now as we know

$$\tilde{i} = \frac{V_0}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$

so,

$$\frac{\tilde{i}_{1/2}}{\sqrt{2}} = \frac{(V_0/R)}{\sqrt{2}} = \frac{V_0}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$

* as $\tilde{i}_{1/2} = V_0/R$

on solving

$$\left(\omega L - \frac{1}{\omega C}\right)^2 = R^2$$

$$\omega L - \frac{1}{\omega C} = \pm R$$

$$\omega^2 LC - 1 = \pm \omega RC$$

$$\omega^2 LC \pm \omega RC - 1 = 0$$

$$\omega = \frac{\pm RC \pm \sqrt{R^2 C^2 + 4LC}}{2LC}$$

as for ω to be positive

$$\sqrt{R^2 C^2 + 4LC} > 0$$

$$\Rightarrow \omega_{1,1/2} = \frac{\sqrt{R^2 C^2 + 4LC} - RC}{2LC}$$

$$\omega_{2,1/2} = \frac{\sqrt{R^2 C^2 + 4LC} + RC}{2LC}$$

$$\text{so, } |\omega_{2,1/2} - \omega_{1,1/2}| = \frac{2RC}{2LC} = R/L$$

$$\text{as, } \omega_0 = \frac{1}{\sqrt{LC}}$$

$$\Rightarrow Q = \frac{1/\sqrt{LC}}{R/L} = \frac{L}{R} \frac{1}{\sqrt{LC}}$$

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

Also, $Q = \frac{V_L \text{ or } V_C \text{ (at resonance)}}{V_0}$

V_0
Source voltage amplitude

We still get

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

Also, $Q = 2\pi \left[\frac{\text{Max energy stored in 1 cycle}}{\text{Energy dissipated in 1 cycle}} \right]$

$$\begin{aligned} \text{max energy stored} &= \frac{1}{2} L \dot{i}_0^2 \\ \text{energy dissipated} &= \left(\frac{1}{2} \right) \dot{i}_0^2 R T \end{aligned} \Rightarrow Q = \frac{2\pi}{T} \frac{L}{R}$$

$$Q = \omega^2 L / R$$


again, $\omega = \frac{1}{\sqrt{LC}}$

so, $Q = \frac{1}{R} \sqrt{\frac{L}{C}}$

as $Q \propto 1/R$

so $R \downarrow \Rightarrow Q \uparrow$ → sharper curve

high current at resonance.

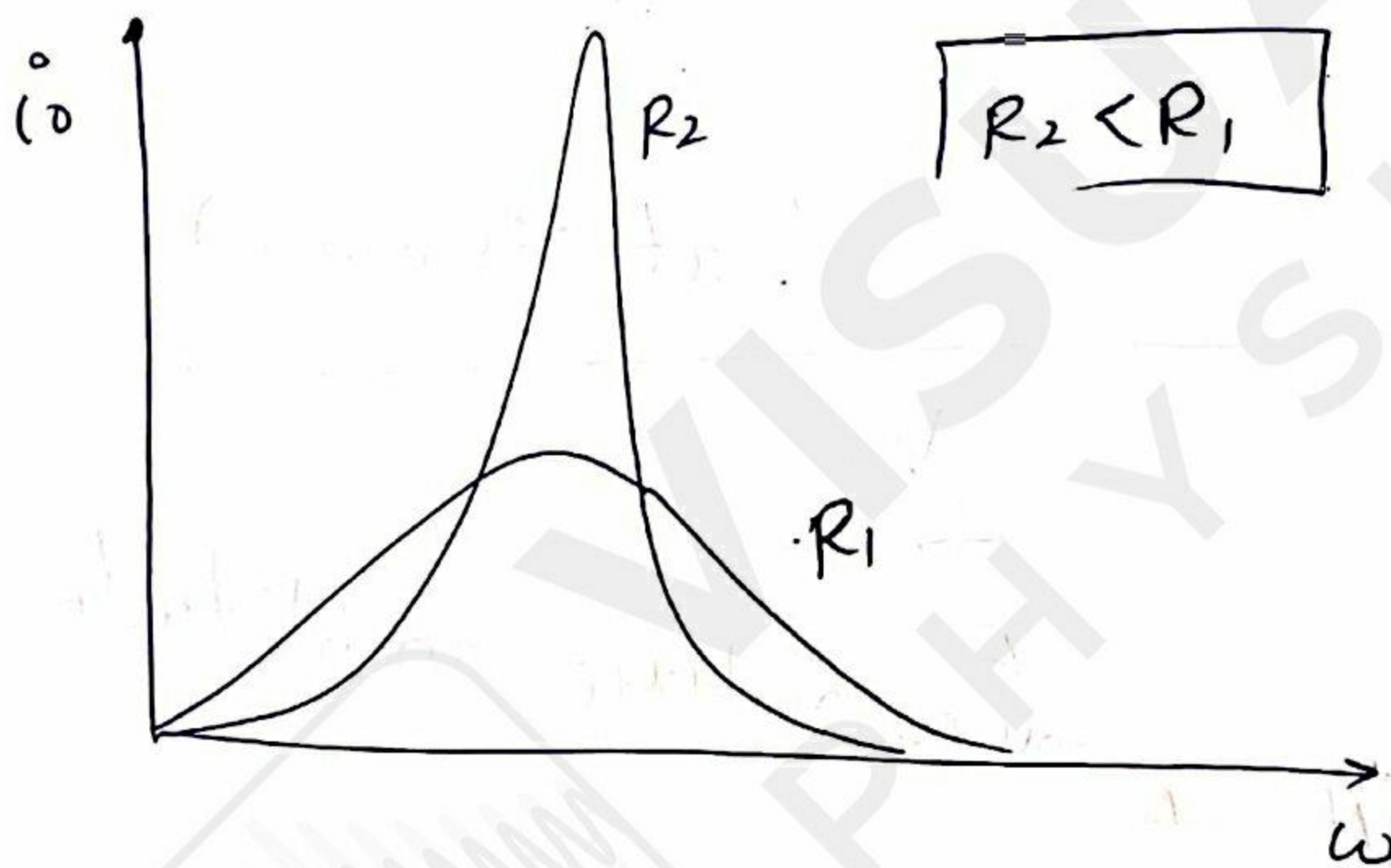

Transformer:

As we know power lost = $i^2 R$

$\Rightarrow$ more the current, more power lost,
now for $(i^2 R)$ loss to reduce we need
to reduce (i) in transmission lines.

* so to reduce power loss $i \downarrow$


As,

$$P_{ac} = V_{rms} \bar{I}_{rms}$$

★ so if $\bar{I}_{rms} \downarrow$ for same P_{ac}
 $V_{rms} \uparrow$

So in transmission, $V_{rms} \uparrow$ so $\bar{I}_{rms} \downarrow$
and when to home again $\bar{I}_{rms} \uparrow$ & $V_{rms} \downarrow$

this is done by transformer

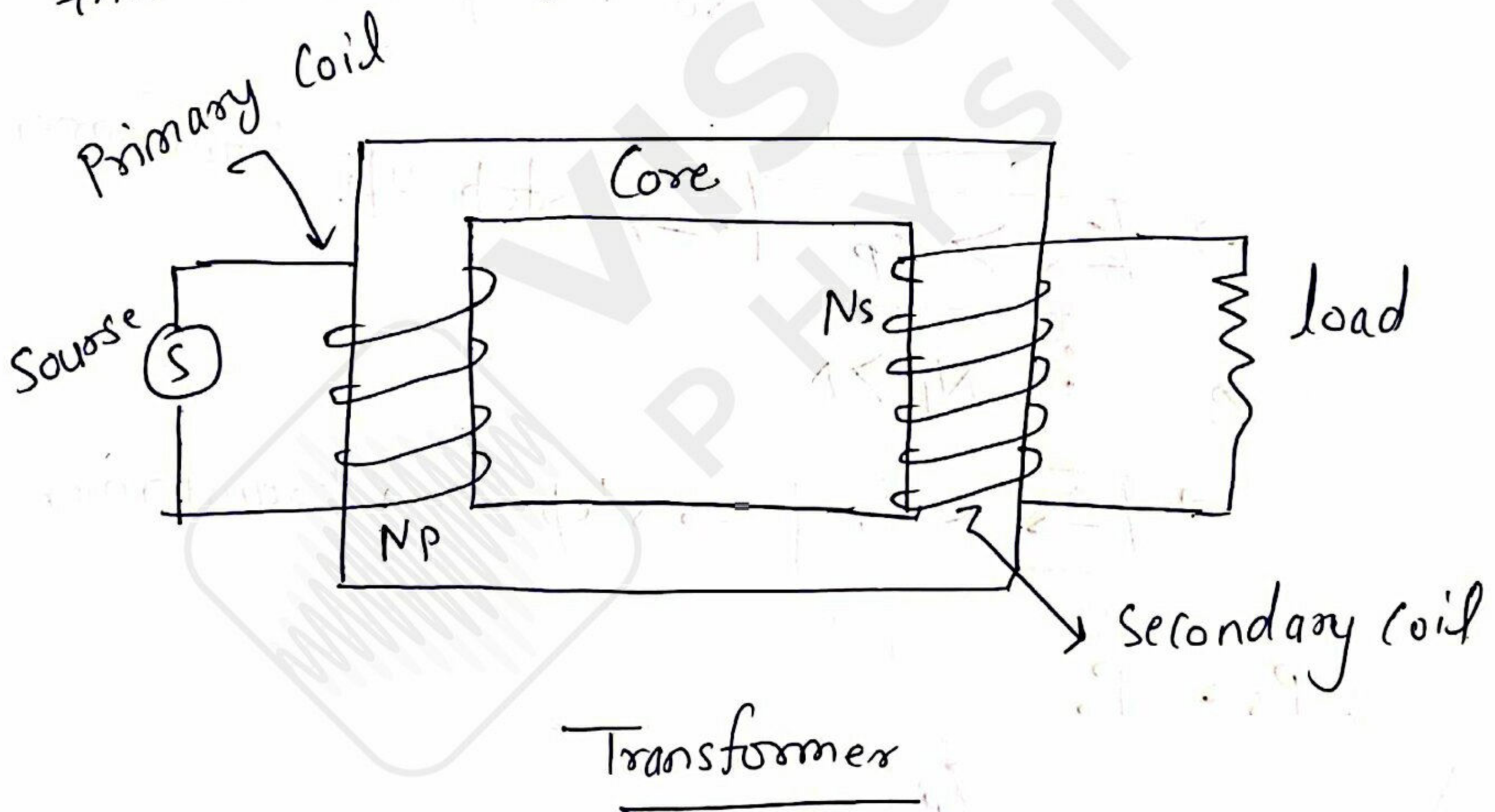

★ now current in primary coil changing and hence flux generated by primary current will change and that changing flux linked with secondary coil through iron core

due to change of flux

$\mathcal{E}_p$ = back emf in primary coil,

$$\Rightarrow \mathcal{E}_p = N_p \frac{d\phi}{dt} \rightarrow \text{flux linked with one turn}$$

* for secondary coil

$$\mathcal{E}_s = N_s \frac{d\phi}{dt}$$

$$\text{so, } \boxed{\frac{\mathcal{E}_p}{\mathcal{E}_s} = \frac{N_p}{N_s}}$$

so if $N_p < N_s$

$$\Rightarrow \boxed{\mathcal{E}_s > \mathcal{E}_p}$$

$\rightarrow$ step up transformer

if $N_p > N_s$

$$\Rightarrow \boxed{\mathcal{E}_s < \mathcal{E}_p}$$

$\rightarrow$ step down transformer

$$P_s = P_p$$

$$\mathcal{E}_s i_s = \mathcal{E}_p i_p$$

$$\Rightarrow \boxed{\frac{i_s}{i_p} = \frac{N_p}{N_s}}$$

so for step up

$$\boxed{i_s \downarrow}$$

and for step down

$$\boxed{i_s \uparrow}$$

Step-up

$\varepsilon_s \uparrow, i_s \downarrow \rightarrow$ used in transmission

Step-down

$\varepsilon_s \downarrow, i_s \uparrow \rightarrow$ used between transmission and household,